

NETWORK

[Kiran-networks-machine]

Syllabus :->

1. BASICS
2. Steady state A.C circuits [Resonance]
3. Theorems.
4. Transients
5. two port network
6. magnetic coupled circuits
7. Graph theory (ESE)
8. Filters (ESE)
9. 3- ϕ circuits. (shifted to power systems)

1) Fundamentals of electric circuits

By Alexander and Sadiku (bit.ly/33IEMRD)

2) Engg. circuit Analysis

By Hayt and Kemmerly.

3) Network Analysis. [conventional method]

By Van Valkenburg.

1) Homework

2) workbook

3) previous papers

GATE $\begin{cases} \rightarrow EE \\ \rightarrow EC \\ \rightarrow IN \end{cases}$


• IAS $\begin{cases} \rightarrow \text{conventional} \\ \rightarrow \text{objective} \end{cases}$

• PSU

• Test series

* Difference between NETWORK AND CIRCUIT:

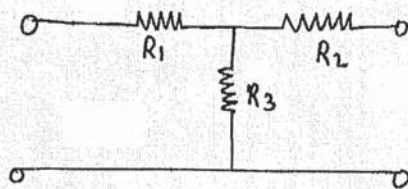Network $\rightarrow$ it is combination of elements, it may or may not consists of closed path, or it may or may not have independent source.




T-Network


EX: (Interview)
(Wireless communication)
(Internet)

Circuit $\rightarrow$

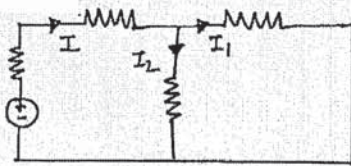it is combination of elements, but it have ~~at least~~ one closed path, or it have at least one independent source



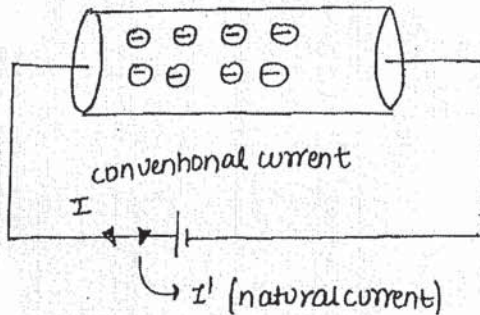EX: (Interview)
(Electrical transmission line)



$$\text{charge of electron} = -1.602 \times 10^{-19} \text{ C}$$

(1) CURRENT (I)

Flow of electron is called current.

(2) $I = \frac{dQ}{dt}$ Rate of change of charge w.r.t to time.

• current Always flows from higher potential to lower potential.

• unit of current $\rightarrow$ C/s or Ampere.

3) $Q = \int_{-\infty}^t I dt = \int_{-\infty}^0 I dt + \int_0^t I dt$

$$Q = Q_0 + \int_0^t I dt$$

(Initial charge)

(3) voltage

emf:- electron move from one point to another point in conductor an force is required. which is called electromotive force.

$$V = \frac{dW}{dQ}$$

$$\begin{aligned} \text{unit} &= \text{J/C} \\ \text{or} \\ \text{unit} &= \text{volts} \end{aligned}$$

(4) power

The time rate of energy is power.

$$P = \frac{dW}{dt} = \frac{dW}{dQ} \cdot \frac{dQ}{dt} = V \cdot I$$

$$P = VI \text{ OR } \frac{V^2}{R} \text{ OR } I^2 R$$

$$P = V^2 G$$


(5) conductance

Reciprocal of Resistance is called conductance.


unit = mho or mmeny

$$G = \frac{1}{R} \text{ (mho) or (ohm)}^{-1}$$

(6) source/sink

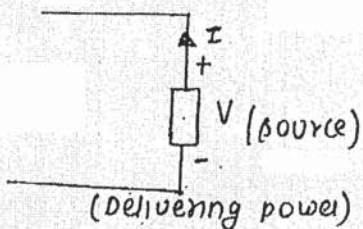

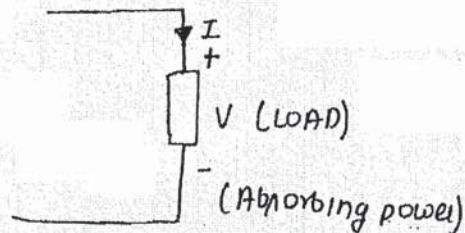Source: current leave from positive terminal




Sink: current enter into positive terminal

Note:

(1) when current is leaving from positive terminal element is (Delivering power).

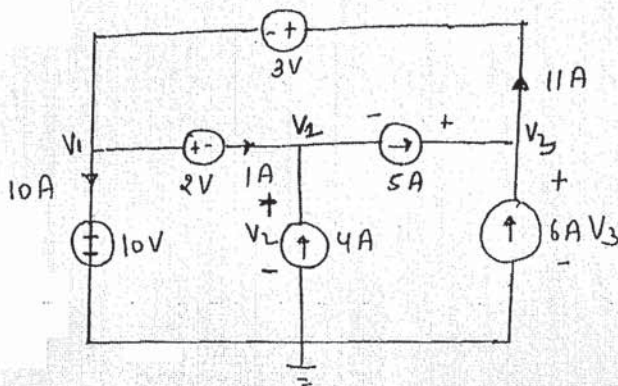(2) when the current is entering from positive terminal element is (Absorbing power).



$$V_1 = 10V$$

$$V_1 - V_2 = 2$$

$$V_2 = 0$$

$$V_2 - V_3 = -3$$

Qw.1 Find power of each element of network shown on left side page?

$$(1) P_{10V} = +10V \times 10 = 100 \text{ (Absorbing power)}$$

$$(2) P_{2V} = 2A \times 1 = 2 \text{ (Absorbing)}$$

$$(3) P_{3V} = 3 \times 11 = 33 \text{ (Absorbing)}$$

$$(4) P_{4A} = 4 \times 8 = 32 \text{ (Delivering)}$$

$$(5) P_{6A} = 6 \times 13 = 78 \text{ (Delivering)}$$

$$(6) P_{5A} = (V_2 - V_3) \times 5A \\ = (8 - 13) \times 5 \\ = -25 \text{ (Absorbing) (Delivering)}$$


$$P_{\text{absorbing}} = 100 + 2 + 33 \\ = 135W$$

$$P_{\text{delivering}} = 78 + 32 + 25 \\ = 135W$$

$$P_{\text{delivering}} = P_{\text{absorbing}}$$

Qw.2

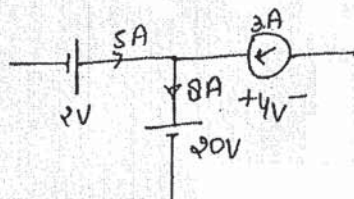Find total power absorbing of figure shown



$$P_{20V} = 8 \times 20 = 160 \text{ (absorb)}$$

$$P_{3A} = 4 \times 3 = 12 \text{ (deliver)} = -12 \text{ (absorb)}$$

$$P_{2V} = 5 \times 2 = 10 \text{ (deliver)} = -10 \text{ (absorb)}$$

$$= 160W - 12W - 10W$$

$$= (160 - 22)W \\ \boxed{138W}$$

Energy

capacity to do work is called Energy.

$$W = \int_0^t P dt$$

$$W = \int_0^t V I dt$$


$$W = P \times t$$

$$W = V I t$$

Joule
or
Watt sec

Ques 3 A fully charged mobile phone is good for 10 min talk time. During talk time, battery delivers a constant current of 2A. Find Energy of battery during talk time.

Ans

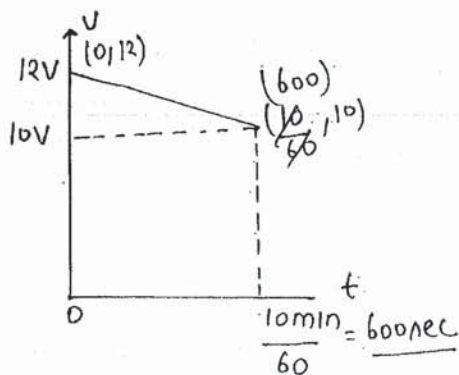

$$(y-12) = \left(\frac{12-10}{-600} \right) \times 600 (x)$$

$$(y-12) = -\frac{2}{150} x$$

$$(V-12) = -12x - \frac{1}{300} t$$

$$V = -12x + 12 - \frac{t}{300} + 12$$

$$\begin{aligned} \text{Energy} &= \int_0^t P dt = \int_0^t V I dt = 2 \int_0^t V dt \\ &= 2 \int_0^{10/60} (-12t + 12) dt \\ &= 2 \times 12 \left[-\frac{t^2}{2} + t \right]_0^{10/60} \\ &= 24 \left[\left(-\frac{1}{6} \right)^2 + \frac{1}{6} \right] \\ &= 24 \left[\frac{1}{6} + \frac{1}{12} \right] \\ &= 2 \int_0^{600} \left(-\frac{t}{300} + 12 \right) dt \\ &= 12 \left[-\frac{t^2}{600} + 12t \right] \\ &= 2 \times 6600 \\ &= 13200 \text{ J} \end{aligned}$$

Method-2

Area method

calculate total Area

$$= \frac{1}{2} [12 + 10] \times 600$$

$$Vt = 6600$$

$$\begin{aligned} \text{Energy} &= VIt \\ &= 6600 \times 2 \\ &= 13200 \end{aligned}$$

$$\approx \boxed{13.2 \text{ kJ}} \quad \checkmark$$

Use Always
time in sec


Note:

$i = Q \times t$ not valid.

$i = \frac{dQ}{dt}$

ALWAYS ONLY USE METHOD-1.

Ques. 4

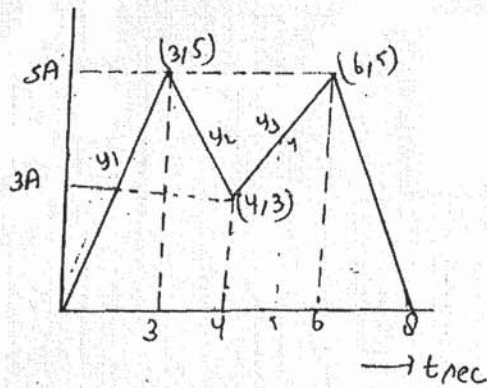

$$y_1 = \frac{5}{3}x \quad y_1 = \frac{5}{3}t$$

$$(y_2 = 3) = -2(t-4)$$

$$y_2 = -2t + 8 + 3$$

$$y_2 = -2t + 11$$

$$(y_3 = 3) = (t-4)$$

$$y_3 = t - 1$$

Find charge measured
by capacitor in 5 sec

$$I = \frac{dQ}{dt}$$

$$dQ = I dt$$

$$dQ = \int_0^3 \frac{5}{3}t + \int_3^4 (-2t + 11) + \int_4^5 (t-1) dt$$

$$\frac{5}{3} \left(\frac{9}{2} \right) + \left(-\frac{2t^2}{2} + 11t \right) \Big|_3^4 + \left(\frac{t^2}{2} - t \right) \Big|_4^5$$

$$= \frac{45}{2} + \left(-\frac{2 \times 4}{2} + 11 \right) + \left(\frac{9}{2} - 1 \right)$$

$$= 7.5 + 4 + 3.5$$

$$= 15 \text{ A}$$

* CLASSIFICATION OF ELEMENTS :->

- (1) Active and passive elements:->
- (2) Linear and non linear
- (3) unidirectional and bidirectional
- (4) Time variant and invariant
- (5) Lumped and Distributed

