

Digital Electronics

Electronics: The study of motion of electron inside a semi-conductor is known as Electronics.


Note: there is a controlled conductivity in the case of semi-conductor

Gate: it is an electronic switching circuit made up of semiconductor switching devices.

Logic gates: Electronic switching ckt i.e. gate with logical ideas implementation by Mr. boolean are logical gates.


Need of digital signal:

Disadvantages of analog signal:

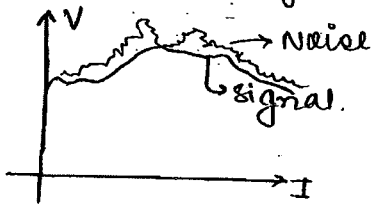

- (a) More bandwidth required.
- (b) More power consumption.
- (c) it is affected by noise more. (at receiving end if we amplify the signal, noise is also amplified)
- (d) no chance for encryption.


Advantages of digital signal:

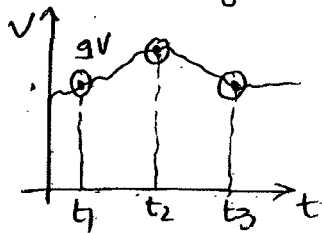

- (a) Less bandwidth required.
- (b) Less power consumption.
- (c) it is affected less by noise.
- (d) encryption is possible in digital signal.

Encryption is using digital data in the form of codes.

Block diagram:

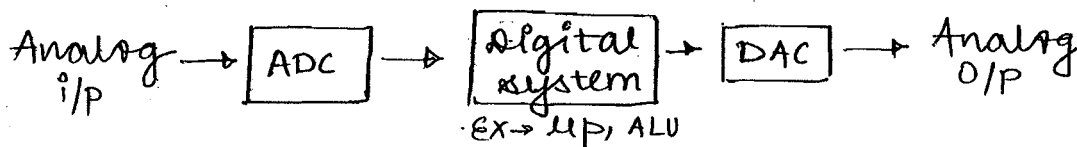

main systems:

- MP
- ALU
- computers
- calculators



subsystems:

- Registers
- flip counters
- flops



Building blocks:

- logic gates
- contains diodes, BJT, mosfet

SYLLABUS

Chapter 1: Basics:

- Boolean algebra
- Logic gates
- K-maps
- Number system
- Codes
- Data representation

Chapter 2: Combinational Circuits:

- Arithmetic circuits
 - half adder, half subtractor, full adder, full subtractor
 - parallel binary adder, look ahead carry adder
 - BCD adder, 2's complement adder subtractor
- Combinational circuits
 - Decoder, multiplexer, Demux, Encoder, decoder
 - comparator, code converter, parity generator, checker

Chapter 3: Sequential Circuits:


- Latches, flipflops, Registers, counters, state machines (mealy morel, moore model)

Chapter 4: Logic Families:

- RTL, DTL, HTL, TTL, ECL
- MOS logic: NMOS, PMOS, CMOS (mainly for Gate Exam)

Chapter 5: ADC and DAC conversions.

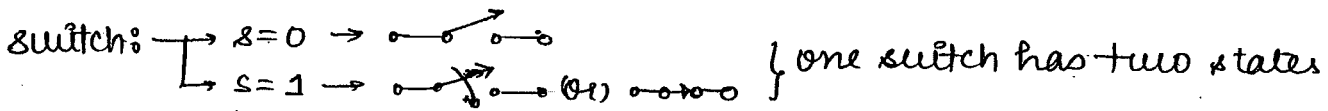Note: for 'n' switches we get 2^n possible states.



S_1	
0	OFF
1	ON

\Rightarrow two switches have four states.

Boolean logical ideas:

These are categorized into three ways:

- \rightarrow two functions that produce constant '0' or '1'. (Null, identity)
- \rightarrow four functions with unary operations; complementary and transfer \hookrightarrow (NOT) \hookrightarrow Buffer.
- \rightarrow ten functions with binary operations. (AND, OR, NAND, NOR, EX-OR, EX-NOR, Inhibition, Implication).

Note: for n input variables, we get (2^n) combinations and (2^{2^n}) possible functions.

Ex = n = 2 $\left[\begin{array}{l} 2^n \rightarrow 2^2 \rightarrow 4 \text{ combinations.} \\ 2^{2^n} \rightarrow 2^{2^2} \rightarrow 16 \text{ functions/operations.} \end{array} \right]$

Truth tables:

X	Y	Null		inhibition		transfer		EX-OR		coincidence	NOT		implication		NAND	Identity
		f_0	f_1	$x \cdot \bar{y}$	$\bar{x} \cdot y$	$x \cdot y$	$\bar{x} \cdot \bar{y}$	$x \oplus y$	\bar{x}		\bar{y}	$x \rightarrow y$	$\bar{x} \rightarrow y$			
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	0	1

$f_0 =$ Null operation

$f_1 = x \cdot y = x \wedge y$ (AND)

$f_2 = x \cdot \bar{y} = x / y = (x \text{ but not } y) \Rightarrow$ inhibition.

$f_3 = x$ transfer \Rightarrow Buffer

$f_4 = \bar{x} \cdot y = y / x = (y \text{ but not } x) \Rightarrow$ inhibition.

$f_5 = y$ transfer \Rightarrow Buffer.

$f_6 = x \oplus y = \bar{x} \cdot y + x \cdot \bar{y} \Rightarrow$ EX-OR (for diff i/p \rightarrow o/p is high)

$f_7 = x + y = x \vee y$

$f_8 = \bar{x} + \bar{y} = x \downarrow y \Rightarrow$ NOR

$f_9 = x \odot y = \bar{x}y + x\bar{y} \Rightarrow$ when i/p same \rightarrow o/p is high
 \Rightarrow coincidence logic gate or Equivalence logic gate.

$f_{10} = \bar{y}$ = complementary = NOT gate.

$f_{11} = x + \bar{y} = x < y =$ if y then x \Rightarrow implication


$f_{12} = \bar{x}$ = complementary = NOT gate.

$f_{13} = \bar{x} + y = x > y =$ if x then y = implication

$f_{14} = (\bar{x} \cdot \bar{y}) =$ NAND = $x \uparrow y$

$f_{15} = 1 =$ Identity.

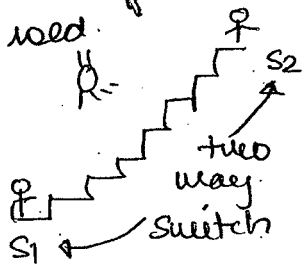note: for staircase and accelerator operation EX-OR logic gate is used.




S_2	S_1	bulb = $S_2 \oplus S_1$
0	0	0
0	1	1
1	0	1
1	1	0

\checkmark Basic logic gates: NOT, AND, OR


\checkmark combinational logic gates: NAND (AND NOT) & NOR (NOT OR)

\checkmark special purpose logic gates: EX-OR, EX-NOR (Arithmetic operations).

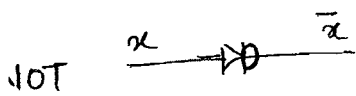• NAND & NOR are said to be universal logic gates.










NOT from NAND

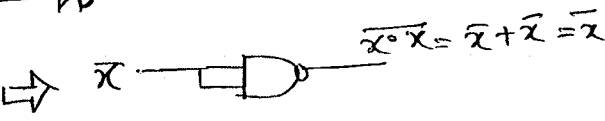


Demorgan's theorem.
 $\bar{x} \cdot \bar{y} = (\bar{x} + \bar{y})$
 $\bar{x} + \bar{y} = (\bar{x} \cdot \bar{y})$

\checkmark symbols:

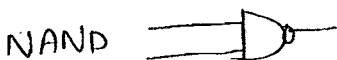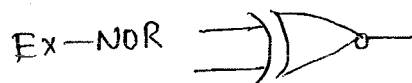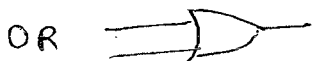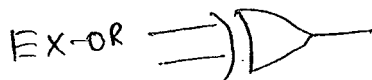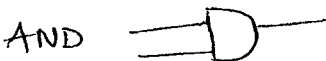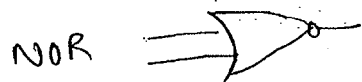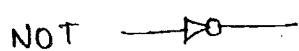

NOT from NOR

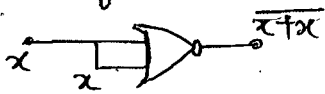

$$\Rightarrow \overline{x+x} = \overline{x \cdot x} = \overline{x}$$

⊛ Shortcut: NO of Nand and NOR gate required:


Gate	NO of Nand gates	NO of NOR gates	NAND to NOR (OR)	NOR to NAND (4)
→ NOT	1	1		
→ AND	2	3	(4)	
→ OR	3	2		
→ EX-OR	4	5		
→ EX-NOR	5	4		

⊛ Design of logic gates using universal logic gates:
 • universal logic gates are NAND and NOR.

(a) NOT from NAND:

- output of NOT $\Rightarrow \overline{x}$
- NO of Nand gates req = 1

Circuit:

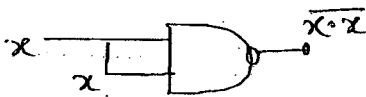


$$\rightarrow \overline{x \cdot x} = \overline{x+x} \Rightarrow \overline{x}$$

(b) AND from NAND:

- output of AND $\Rightarrow x \cdot y$
- NO of NAND req = 2


Circuit

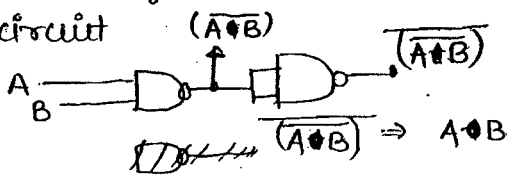

$$\overline{\overline{A \cdot B}} \Rightarrow A \cdot B$$

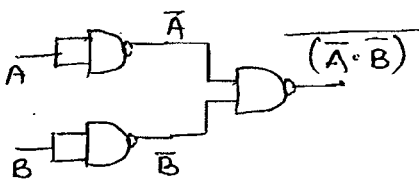(c) OR from NAND:

- output of OR $\Rightarrow x+y$
- NO of NAND $\Rightarrow 3$



$$\rightarrow \overline{\overline{A} \cdot \overline{B}} \Rightarrow \overline{\overline{A+B}} = A+B$$

(d) NOT from NOR:

- output of NOT gate $= \overline{x}$
- NO of NOR gates req = 1


Circuit:



$$\rightarrow \overline{x+x} = \overline{x \cdot x} = \overline{x}$$

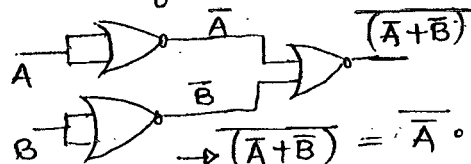(e) AND from NOR:


- output of AND $= x \cdot y$
- NO of NOR req = 3



$$\rightarrow \overline{\overline{A} + \overline{B}} = \overline{\overline{A \cdot B}} = A \cdot B$$

(f) OR from NOR:

- output of OR $= x+y$
- NO of NOR = 2

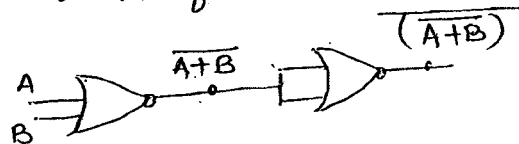


$$\rightarrow \overline{\overline{A+B}} = A+B$$

g) XOR from NAND: $(A \oplus B)$

→ output of EX-OR = $\bar{A}B + A\bar{B}$

→ no. of NAND = 4

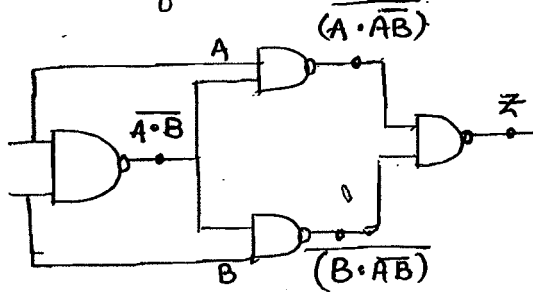

$$Z = \overline{(A \cdot \bar{A}B) \cdot (B \cdot \bar{A}B)}$$

$$Z = \overline{(A \cdot \bar{A}B)} + \overline{(B \cdot \bar{A}B)}$$

$$Z = A \cdot \bar{A}B + B \cdot \bar{A}B$$

$$Z = A \cdot (\bar{A} + B) + B \cdot (\bar{A} + B)$$

$$Z = A \cdot \bar{A} + A \cdot B + B \cdot \bar{A} + B \cdot B$$


$$Z = A\bar{B} + B\bar{A}$$

$$Z = A\bar{B} + \bar{A}B = A \oplus B$$

h) EX-NOR from NAND: $(A \odot B)$

→ output of EXNOR = $\bar{A}\bar{B} + AB$

→ no. of NAND req = 5

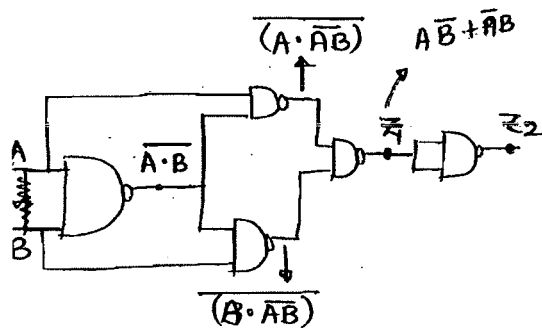

$$Z_1 = A\bar{B} + \bar{A}B$$

$$Z_2 = \bar{Z}_1$$

$$= \overline{(A\bar{B} + \bar{A}B)}$$

$$= \overline{A\bar{B}} \cdot \overline{\bar{A}B}$$

$$= (\bar{A} + B)(A + \bar{B})$$

$$= \bar{A}(A + \bar{B}) + B(A + \bar{B})$$


$$= A\bar{A} + \bar{A}\bar{B} + BA + B\bar{B}$$

$$Z_2 = \bar{A}\bar{B} + AB$$

(h) EX-OR from NOR:

→ output of EX-OR = $\bar{A}B + A\bar{B}$

→ no. of NOR = 5

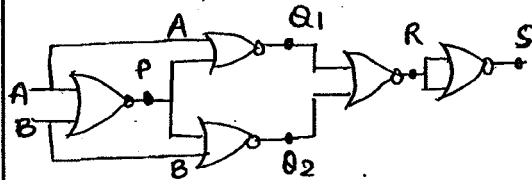

$$P = (\bar{A} + \bar{B})$$

$$Q_1 = (\bar{A} + P) = \overline{\overline{A + (\bar{A} + \bar{B})}} = \bar{A} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{A} \cdot (A + B)$$

$$Q_2 = (\bar{B} + P) = \overline{\overline{B + (\bar{A} + \bar{B})}} = \bar{B} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{B} \cdot (A + B)$$

$$R = (Q_1 + Q_2) = \overline{\overline{(\bar{A} \cdot (A + B) + \bar{B} \cdot (A + B))}}$$

$$= \overline{\overline{(\bar{A}A + \bar{A}B + \bar{B}A + \bar{B}B)}} = \overline{\overline{(\bar{A}B + \bar{B}A)}}$$


$$R = (\bar{A}B + \bar{B}A)$$

$$S = \bar{R} = \overline{(\bar{A}B + \bar{B}A)} = \bar{A}B + \bar{B}A$$

(j) EX-NOR from NOR:

→ output of EXNOR = $\bar{A}\bar{B} + AB$

→ no. of NOR = 4

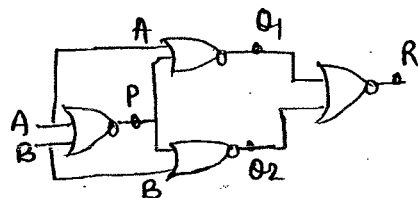

$$P = (\bar{A} + \bar{B})$$

$$Q_1 = (\bar{A} + P) = \overline{\overline{A + (\bar{A} + \bar{B})}} = \bar{A} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{A} \cdot (A + B) = A\bar{A} + \bar{A}B = \bar{A}B$$

$$Q_2 = (\bar{B} + P) = \overline{\overline{B + (\bar{A} + \bar{B})}} = \bar{B} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{B} \cdot (A + B) = \bar{B}A + \bar{B}B = \bar{B}A$$

$$R = (\bar{A}B + \bar{B}A)$$



$$= \bar{A}B \cdot \bar{B}A$$

$$= (\bar{A} + \bar{B}) \cdot (A + B)$$


$$= (\bar{A} + \bar{B}) \cdot (A + B)$$

$$= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})$$

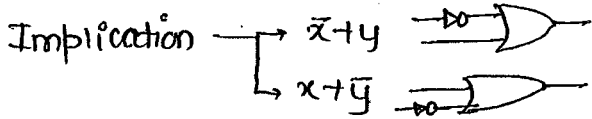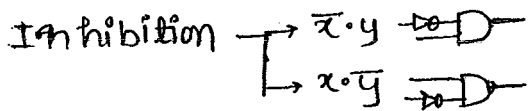
$$= A\bar{A} + A\bar{B} + B\bar{A} + B\bar{B}$$



these are also universal logic gates.

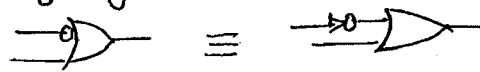


switching circuits as logic gates:

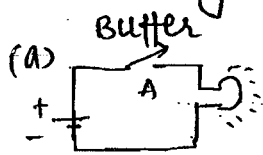


A	bulb
0	off (0)
1	ON (1)

$f = A$
(Buffer)

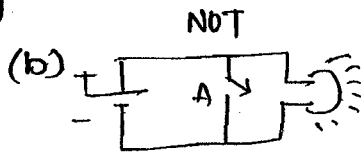


A	bulb
0	ON (1)
1	off (0)

$f = \bar{A}$
(NOT)

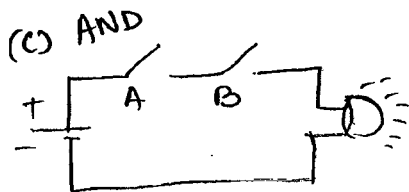


A	B	bulb
0	0	0
0	1	0
1	0	0
1	1	1

$f = A \cdot B$
(AND)

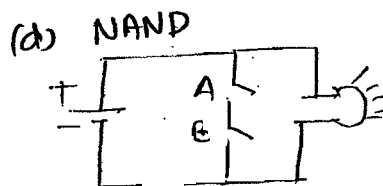


A	B	bulb
0	0	1
0	1	1
1	0	1
1	1	0

$f = \overline{A \cdot B}$
= NAND.

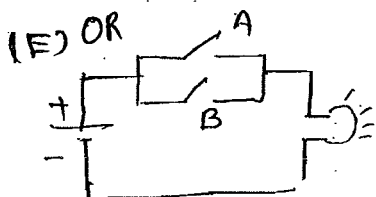


A	B	bulb
0	0	0
0	1	1
1	0	1
1	1	1

$f = A + B$
(OR)

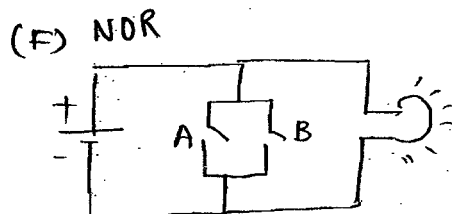

A	B	bulb
0	0	1
0	1	0
1	0	0
1	1	0

$f = \overline{A + B}$
= NOR

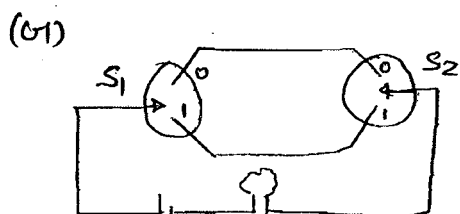


S ₁	S ₂	bulb
0	0	1
0	1	0
1	0	0
1	1	1

$f = S_1 \oplus S_2$


⇒ workbook practice : CH2 : Q T1, T2

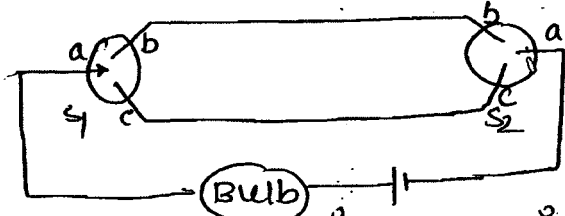Q1 A two way switch has three terminals a, b and c. In on position (logic value 1), a is connected to b, and in off position a is connected to c. Two of these switches are connected to bulb as shown in figure:



Which of the following expression, if true, will always result in lighting of bulb?

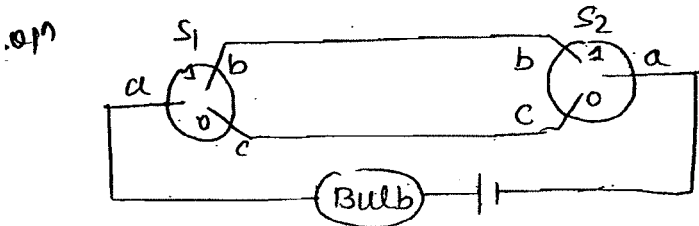- (a) $s_1 \cdot \bar{s}_2$ (b) $s_1 + s_2$ (c) $\overline{s_1 \oplus s_2}$ (d) $s_1 \oplus s_2$







s_1	s_2	bulb
0	0	1
0	1	0
1	0	0
1	1	1

} $s_1 \oplus s_2$

$$s_1 \oplus s_2 = \overline{s_1 \oplus s_2}$$

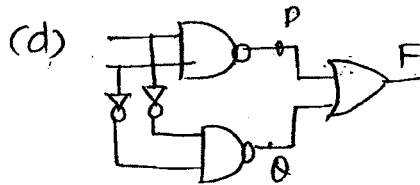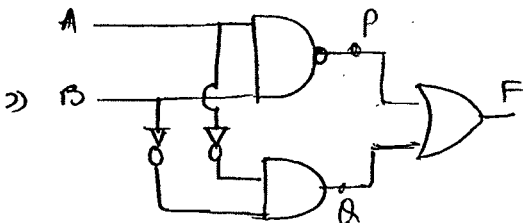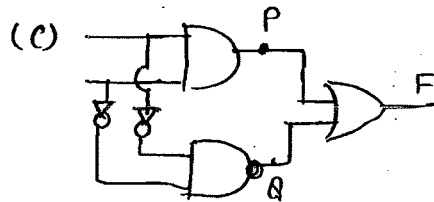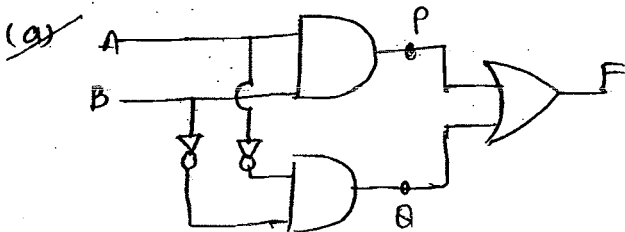Q2 which one of the following represents coincidence logic gate?




Q1) (a) truth table

A	B	P	Q	F
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

} $s_1 \oplus s_2 \rightarrow$ coincidence logic gate

Qex:

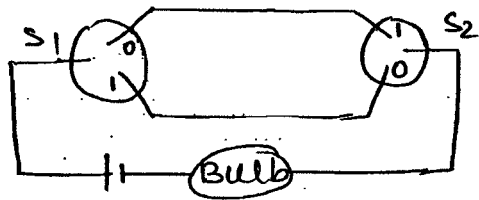

S1	S2	bulb
0	0	0
0	1	1
1	0	1
1	1	0

} $S_1 \oplus S_2$

* canonical forms:

x	y	min term	(product term)
m ₀	0	0	$\bar{x} \cdot \bar{y}$
m ₁	0	1	$\bar{x} \cdot y$
m ₂	1	0	$x \cdot \bar{y}$
m ₃	1	1	$x \cdot y$

$f(x,y) = \sum m(1,3)$

SOP

x	y	max term	(sum term)
M ₀	0	0	$x+y$
M ₁	0	1	$x+\bar{y}$
M ₂	1	0	$\bar{x}+y$
M ₃	1	1	$\bar{x}+\bar{y}$



$f(x,y) = \prod M(0,2)$

POS

$$\Rightarrow \overline{\bar{x} \cdot \bar{y}} = \overline{\bar{x}} + \overline{\bar{y}} = x + y$$

i.e. (min term) = (max term)
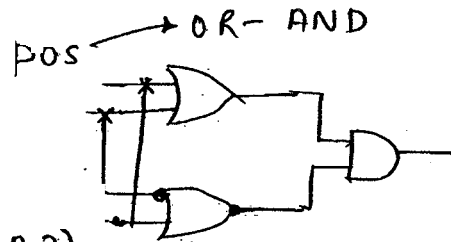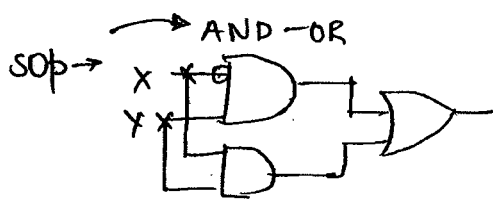
$$\begin{cases} \bar{m}_0 = M_0 & \bar{m}_1 = M_1 \\ \bar{m}_2 = M_2 & \bar{m}_3 = M_3 \end{cases}$$



$$f = \sum m(1,3) = \prod M(0,2)$$

missing no. ↑

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

SOP = ?
POS = ?

$$\begin{aligned} \text{SOP}(f) &= \bar{x}y + x\bar{y} \\ \text{POS}(f) &= (\bar{x} + \bar{y})(x + y) \\ &= \bar{x}(x+y) + \bar{y}(x+y) \\ &= \bar{x}\bar{x} + \bar{x}y + \bar{y}x + \bar{y}\bar{y} \\ &= \bar{x}y + x\bar{y} = x \oplus y \end{aligned}$$

} This is EX-OR gate

• In canonical SOP form, each product term must contain all variable of given expression.

Note: In canonical SOP, each product term is known as min term.

• In canonical POS, each sum term is known as max term.

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

SOP = ?
POS = ?

$$\begin{aligned}
 \text{SOP}(f) &= x \cdot y \\
 \text{POS}(f) &= (x+y)(x+\bar{y})(\bar{x}+y) \\
 &= (x+y)[x(\bar{x}+y) + \bar{y}(\bar{x}+y)] \\
 &= (x+y)(x\bar{x} + xy + \bar{y}\bar{x} + y\bar{y}) \\
 &= (x+y)(0 + xy + \bar{y}\bar{x} + 0) \\
 &= (x+y)(xy + \bar{y}\bar{x}) \\
 &= x(xy + \bar{y}\bar{x}) + y(xy + \bar{y}\bar{x}) \\
 &= xy + \bar{y}\bar{x} + yx + \bar{y}\bar{y} \\
 &= xy + \bar{y}\bar{x} + yx + 0 \\
 &= xy + \bar{y}\bar{x} + yx \\
 &= x \cdot y
 \end{aligned}$$

NOTE: In the min term zero corresponding variable is complemented and one corresponding variable is taken without complementation.

In the case of max term, 0 corresponding variable is taken without complementation & 1 corresponding variable is taken with complementation.

$$\begin{aligned}
 f &= \bar{x} \cdot y + x \cdot y \rightarrow \text{canonical sop} \\
 &\quad \downarrow \quad \downarrow \\
 &\quad \frac{01}{1} \quad \frac{11}{3}
 \end{aligned}$$

$$f = \sum m(1,3) \rightarrow \text{standard form}$$

$$\begin{aligned}
 f &= \bar{x} \cdot y + x \cdot y \\
 &= xy(\bar{x} + x) \\
 &= y(1) \\
 &= y \rightarrow \text{minimal form}
 \end{aligned}$$

	x	y	f
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0

} find SOP & POS:
 → canonical form
 → standard form
 → minimal form

SOP: $f = \sum m(0,2) \rightarrow \text{standard form}$

$$f = m_0 + m_2$$

$$= \bar{0}0 \cdot \bar{1}0$$

$$f = \bar{x}\bar{y} + x\bar{y} \rightarrow \text{canonical form}$$

$$= \bar{y}(\bar{x} + x)$$

$$= \bar{y}(1)$$

$$f = \bar{y} \rightarrow \text{minimal form.}$$

Pos: $f = \pi M(1, 3) \rightarrow$ ~~can~~ standard form.

$$= M_1 + M_3$$

$$f = x\bar{y} + x\bar{y} \rightarrow \text{canonical form.}$$

$$= \bar{y}(x + \bar{x})$$

$$f = \bar{y} \rightarrow \text{minimal form.}$$

① If more zero's is given in output function then we go for min term with (1)

If more 1's are given in output function then we go for max term with (0).

$$f = \sum m(1, 5) = \pi M(0, 2, 3, 4, 6, 7)$$


$\rightarrow 101 \rightarrow n=3 \rightarrow 2^3 = 8 \text{ combinations}$

$$= \pi M(1, 9) = \sum m(0, 2, 3, 4, 5, 6, 7, 8, 9, 11, 12, 13, 14, 15)$$

1001
 \downarrow
 $n=4$
 $\hookrightarrow 2^4 = 16 \text{ combinations.}$

Ex: $f_1 = \sum m(0, 1, 2, 4)$
 $f_2 = \sum m(1, 3, 4, 5)$
 $f_3 = \sum m(2, 3, 4, 5, 6, 7)$

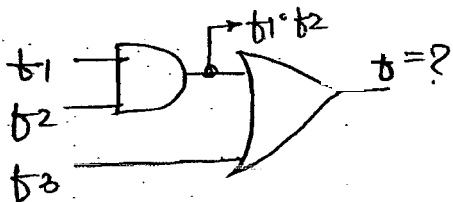
AND = $f_1 \cdot f_2 = f_1 \cap f_2$
 OR = $f_1 + f_2 = f_1 \cup f_2$



$f_1 \cdot f_2 = \sum m(1, 4)$
 $f_3 = \sum m(2, 3, 4, 5, 6, 7)$

$f \Rightarrow$
 $f_1 \cdot f_2 = \sum m(1, 2, 3, 4, 5, 6, 7)$
 $\neq f_3$

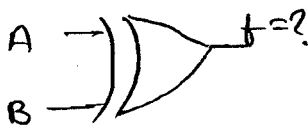Ex: $A = \sum m(0, 1, 4, 5)$
 $B = \sum m(2, 3, 4, 5, 6, 7)$



$f = A \oplus B$
 $= \bar{A}\bar{B} + A\bar{B} + \bar{A}B + AB$
 $= (\bar{A} + B)A + (\bar{A} \cdot B)$
 \neq

$\bar{A}B \rightarrow$ inhibition $\rightarrow B$ but not A .
 $\bar{A}B = \sum m(2, 3, 6, 7)$




$A\bar{B} \rightarrow$ inhibition $\rightarrow A$ but not B .
 $A\bar{B} = \sum m(0, 1)$

$\bar{A}B + A\bar{B} = \sum m(0, 1, 2, 3, 6, 7)$

workbook practice: CH2: Q 2)

21 A universal logic gate can be implemented any boolean function by connecting sufficient no. of them appropriately.

These gates shown:

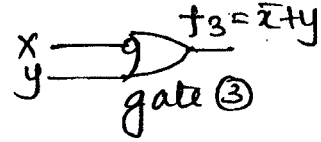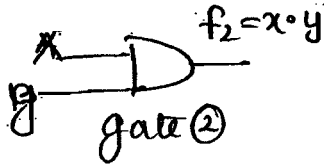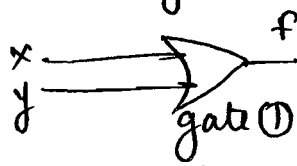


which of the following is correct statement?

- (a) Gate 1 is a universal gate.
- (b) Gate 2 is a universal gate.
- (c) Gate 3 is a universal gate.
- (d) Gate none of the gates are universal gate.



soln) Gate 1: $f_1 = x + y \rightarrow$ it is OR gate \rightarrow not universal.

Gate 2: $f_2 = x \cdot y \rightarrow$ it is AND gate \rightarrow not universal.

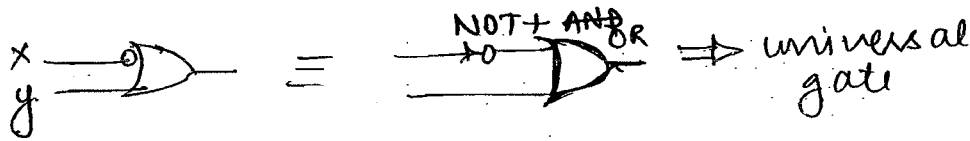Gate 3: $f_3 = \bar{x} + y \rightarrow$ implication \rightarrow universal gate.




Alternative logic gates:

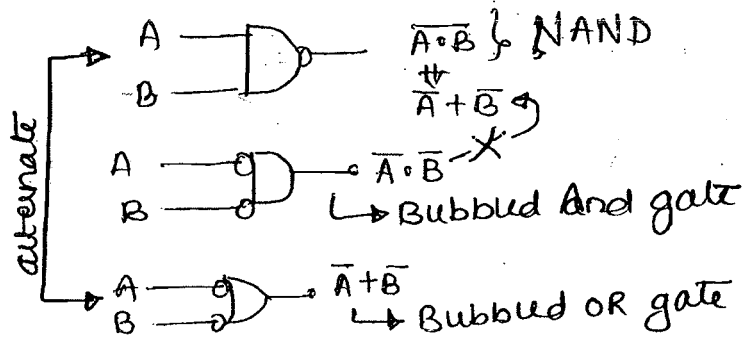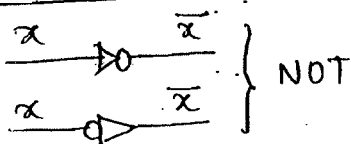

- NAND $\xrightarrow{\text{alternate}}$ Bubbled OR gate
 - NOR $\xrightarrow{\text{alternate}}$ Bubbled AND gate
 - AND $\xrightarrow{\text{alternate}}$ Bubbled NOR gate
 - OR $\xrightarrow{\text{alternate}}$ Bubbled NAND gate
- } shortcut.

⇒ workbook practice: CH2: Q3, Q1, Q12

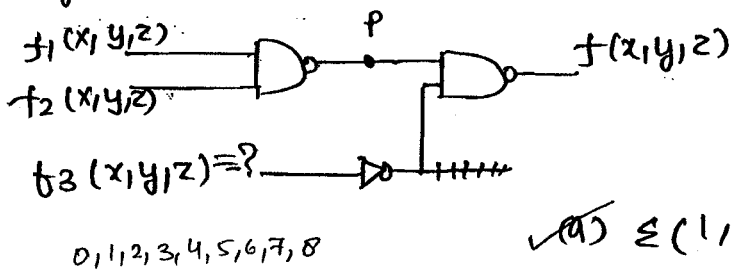Q3 consider the following logic circuit whose inputs are functions f_1, f_2 and f_3 and output is f . given that:



$$f_1(x,y,z) = \sum(0,1,3,5)$$

$$f_2(x,y,z) = \sum(6,5)$$

$$f(x,y,z) = \sum(1,4,5)$$

f_3 is

0,1,2,3,4,5,6,7,8

✓ (a) $\sum(1,4,5)$

(b) $\sum(6,7)$

(c) $\sum(0,1,3,5)$

(d) None.



Solⁿ

$$P = \overline{f_1 \cdot f_2} = \overline{f_1} + \overline{f_2}$$

$$= \sum(2,4,6,7,8) + \sum(1,2,3,4,7,8)$$

$$= \sum(1,2,3,4,6,7,8)$$

X

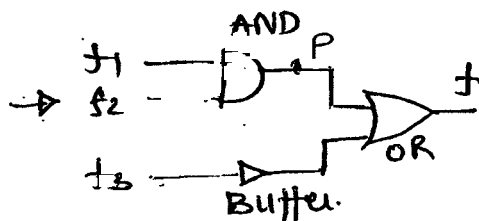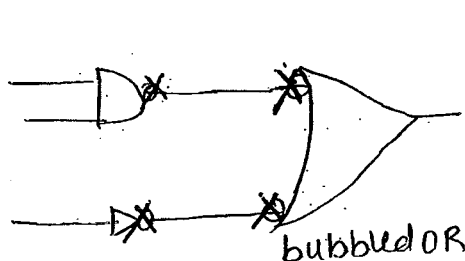

$$P = f_1 \cdot f_2 = f_1 \cap f_2$$

$$P = \sum m(5)$$

$$f_3 = \sum m(1,4,5)$$

$$f = P \cup f_3$$

$$\sum m(1,4,5) = \sum m(5) \cup \sum m(\text{---})$$

$$\therefore f_3 = \sum m(1,4,5) \text{ or } \sum m(1,4)$$

Q1 consider the following SOP expression F;

$$F = ABC + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + \overline{A}\overline{B}\overline{C}$$

the equivalent ~~sum of product~~ product of sum expression is:

✓ (a) $F = (A+B+C) (\overline{A}+B+C) (\overline{A}+\overline{B}+C)$

(b) $F = (A+\overline{B}+\overline{C}) (A+B+C) (\overline{A}+\overline{B}+\overline{C})$

(c) $F = (\overline{A}+B+\overline{C}) (A+\overline{B}+\overline{C}) (A+B+C)$

(d) $F = (\overline{A}+\overline{B}+C) (A+B+\overline{C}) (A+B+C)$

Solⁿ: $f = ABC + \bar{A}\bar{B}C + A\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C}$

minterms: $\downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow$
 $\begin{matrix} 111 & 001 & 001 & 011 & 000 \\ \downarrow 7 & \downarrow 1 & \downarrow 5 & \downarrow 3 & \downarrow 0 \end{matrix}$

done without teacher's logic good*

$f = \sum m(0, 1, 3, 5, 7)$
 $f = \prod M(2, 4, 6)$

$2 \rightarrow 010 \rightarrow A + \bar{B} + C$
 $4 \rightarrow 100 \rightarrow \bar{A} + B + C$
 $6 \rightarrow 110 \rightarrow \bar{A} + \bar{B} + C$


maxterms: $f = (A+B+C)(\bar{A}+B+C)(\bar{A}+\bar{B}+C)$

12 statement (I): A NAND gate represents universal logic gate.
 statement (II): only two NAND gates are sufficient to accomplish all basic gates.

Ans statement (I) -> true
 statement (II) -> false. } option (C) statement (I) is true but statement (II) is false.

9 NAND and NOR gates are universal gates because:

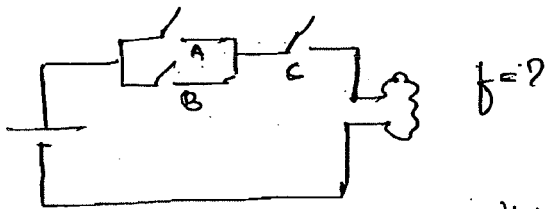
- (a) they are available everywhere
- (b) they are widely used in IC packages.
- (c) they can be combined to produce AND, OR & NOT gate
- (d) they can be manufactured easily.




bulb (1) $\Rightarrow A=1, C=1, B$ don't care
 $\Rightarrow B=1, C=1, A$ don't care

	A	B	C	f
(5)	1	0	1	1
(7)	1	1	1	1
(3)	0	1	1	1
(7)	1	1	1	1

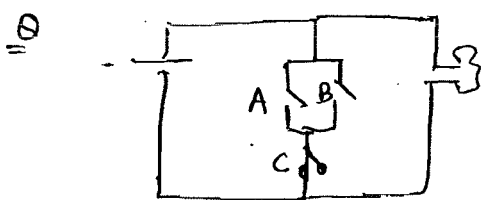$f = \sum m(3, 5, 7)$
 $f = (A \cdot \bar{B} \cdot C) + (\bar{A} B C) + (A B C)$
 $f = (A+B) \cdot C$







$f = (A+B) \cdot C$

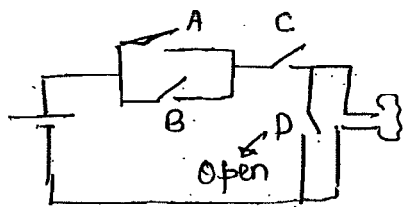

$$f = AC\bar{D} + BC\bar{D}$$

$$f = C\bar{D}(A+B)$$

⊛ Positive and negative logic

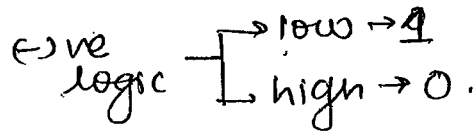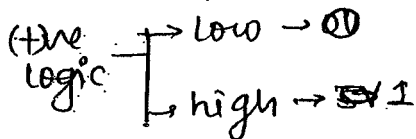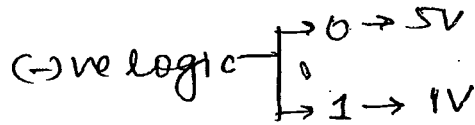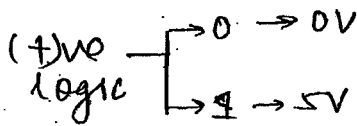

High: low → (+)ve logic
-2V, -7V
1 0

(+)ve And logic:

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

(-)ve And logic

x	y	AND(-ve)
0	0	1
0	1	1
1	0	1
1	1	0

(+)ve OR logic.

(+)ve AND \equiv (-ve) OR & vice versa.
 (+)ve NAND \equiv (-ve) NOR & vice versa.

⊛ Duality

$$B = \{0, 1\}$$

$$B = \{0, 1\}$$

Boolean laws are maintaining duality.

Step 1: Interchange {0, 1} AND \leftrightarrow OR
 Step 2: Interchange 0, 1.

EX $x \cdot 0 = 0$ ✓
 $x + 1 = 1$ ✓ } Boolean laws are valid in duality.

$$f = A + B \cdot \bar{C}$$

$$f^D = A \cdot (B + \bar{C})$$

$$(f^D)^D = A + (B \cdot \bar{C}) = f$$

AND	OR
$x \cdot x = x$	$x + x = x$
$x \cdot 0 = 0$	$x + \bar{x} = 1$
$x \cdot 1 = x$	$x + 0 = x$
$x \cdot \bar{x} = 0$	$x + 1 = 1$

$\rightarrow (f^D)^D = f \rightarrow$ it happens for every boolean expression.

if $f^D = f \rightarrow f$ is self dual

Ex = $f = AB + BC + CA$

$f^D = (A+B) \cdot (B+C) \cdot (C+A)$

$f^D = [AB + AC + BB + BC] \cdot (C+A)$

$= (AB + AC + BC + BB)(C+A)$

$f^D = BC + AB + AC$ (on solving) $= f$.

} f is self dual.

checking of self duality:

- conditions: \rightarrow it should be a natural function.
 \rightarrow it should not contain mutually exclusive terms.

natural functions:

x	y	z	f (given)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

min terms = m_2, m_4, m_5, m_7

max terms = M_0, M_1, M_3, M_6

[natural is no of min terms = no of max terms]
function

mutually exclusive terms:

x	y	z	(0,7)	(1,6)	(2,5)	(3,4)
\rightarrow 0	0	0	\nmid	\nmid	\nmid	\nmid
\rightarrow 0	0	1	\nmid	\nmid	\nmid	\nmid
\rightarrow 0	1	0	\nmid	\nmid	\nmid	\nmid
\rightarrow 0	1	1	\nmid	\nmid	\nmid	\nmid
\rightarrow 1	0	0	\nmid	\nmid	\nmid	\nmid
\rightarrow 1	0	1	\nmid	\nmid	\nmid	\nmid
\rightarrow 1	1	0	\nmid	\nmid	\nmid	\nmid
\rightarrow 1	1	1	\nmid	\nmid	\nmid	\nmid

$2 \times 2 \times 2 \times 2 = 16$

mutually exclusive terms:
 $0 \rightarrow 000$
 $7 \rightarrow 111$ } (0,7) are mutually exclusive terms

$1 \rightarrow 001$
 $6 \rightarrow 110$ } (1,6)

$2 \rightarrow 010$
 $5 \rightarrow 101$ } (2,5)

$3 \rightarrow 011$
 $4 \rightarrow 100$ } (3,4)

$\therefore f = \sum (m(0,1,2,5))$

f is natural (min term = max term)

f is mutually exclusive \rightarrow so it is not self dual.

note: no of possible self dual forms = $2^{2^n - 1}$ (provided that it should be a natural function/form).

for mutually Exclusive terms:

$$\begin{cases} \text{if } n=2 & \text{sum of terms} = 3 \\ \text{if } n=3 & \text{sum of terms} = 7 \\ \text{if } n=4 & \text{sum of terms} = 15 \end{cases} \left\{ \begin{array}{l} \text{for mutually exclusive} \\ \text{terms, sum of terms} = (2^n - 1) \end{array} \right.$$

Ex = $f_1 = \Sigma m(0,1,4) \rightarrow$ not self dual.

$f_2 = \Sigma m(2,3,4,5) \rightarrow$ not self dual.

$f_3 = \Sigma m(0,1,2,3,4) \rightarrow$ self dual.

⇒ workbook practice: CH2: Q2, 23

Q22 for the identity $AB + AC + BC = AB + AC$, the dual form is

(a) $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C) \checkmark$

(b) $(\bar{A}+\bar{B})(A+\bar{C})(\bar{B}+\bar{C}) = (\bar{A}+\bar{B})(A+\bar{C})$

(c) $(A+B)(\bar{A}+C)(B+C) = (\bar{A}+\bar{B})(A+\bar{C})$

(d) $\bar{A}\bar{B} + A\bar{C} + \bar{B}\bar{C} = \bar{A}\bar{B} + A\bar{C}$

Q21ⁿ $AB + \bar{A}C + BC = AB + \bar{A}C$ { $\cdot, +$ } \rightarrow interchange \rightarrow { $0, 1$ }
 $(\bar{A}+\bar{B}) \cdot (\bar{A}+\bar{C}) \cdot (\bar{B}+\bar{C}) = (\bar{A}+\bar{B})(\bar{A}+\bar{C})$

Q23 The dual form of a boolean function $F(x_1, x_2, \dots, x_n, +, \cdot, \bar{})$, written as F^D , is the same expression as that of F with $+$ and \cdot swapped. F is said to be self dual if $F = F^D$. The no. of self dual functions with n boolean variables is:

(a) 2^n

(c) 2^{2^n}

(b) $2^{2^n - 1}$

(d) $2^{2^n - 1}$

⇒ If $n=1$
 $f = A$
 $f^D = A$ ①
 $f = \bar{A}$
 $f^D = \bar{A}$ ②
 } no. of possible self dual functions
 $= 2^{2^n - 1} = 2^{2^1 - 1} = 2^{2^0} = 2$

⊗ complementing a boolean expression:

$f = A + B \cdot \bar{C}$

$\bar{f} = ?$


$f^D = A \cdot (B + \bar{C})$

$\bar{f} = \bar{f^D} = \bar{A} \cdot (\bar{B} + C) \checkmark$

→ step ①: dual form

→ step ②: complement the individual variables.


* Degenerative forms:

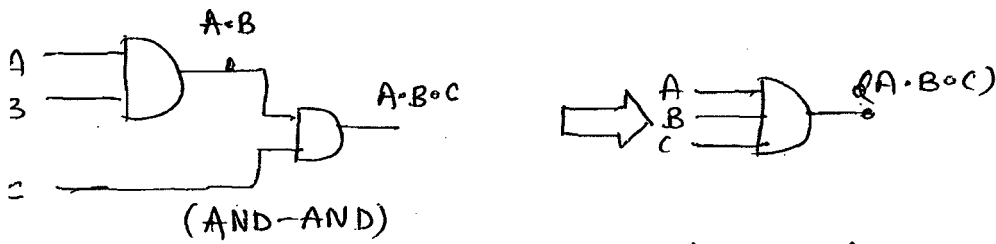


AND-AND is a degenerated form for AND gate.

if a two level logic gate system o/p is expressed with a single logic gate then that two level logic gate system is known as degenerated form for that single logic gate.

Non degenerative form:

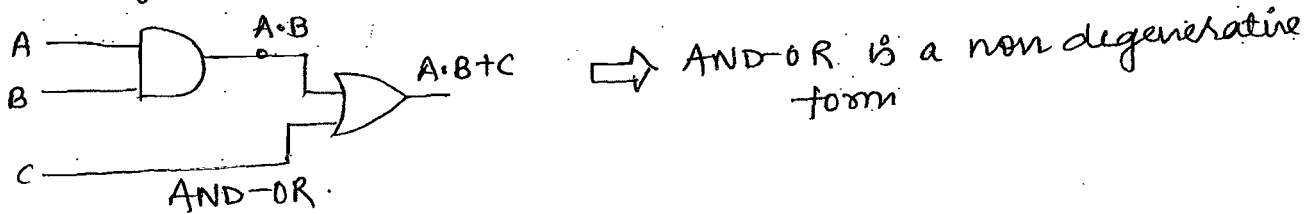

Non degenerative form list: (Shortcut):

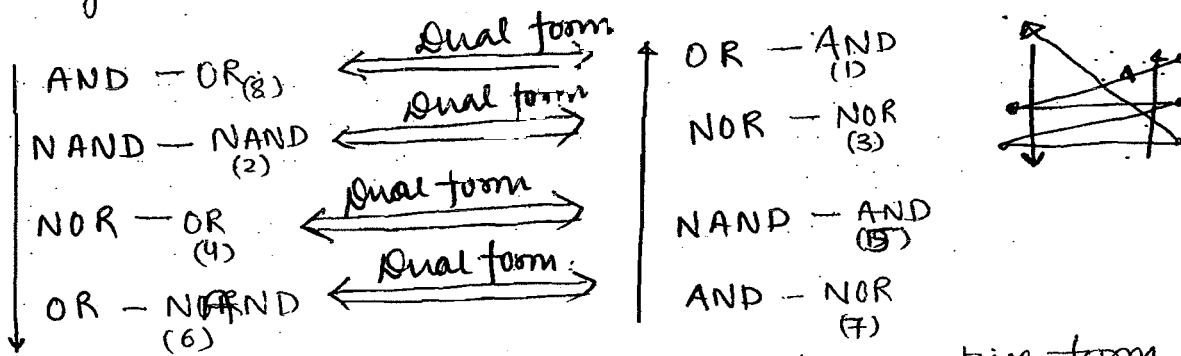

In the above representation of non degenerative form combinations present in the same row are dual forms

Ex $f = AB + C$
AND-OR



$f^D = (A+B) \cdot C$
OR-AND




AND-OR $\xleftrightarrow{\text{dual}}$ OR-AND

⇒ EX-OR: shortcut:

x	y	f = x ⊕ y
0	0	0
0	1	1
1	0	1
1	1	0

$$f = x \oplus y = \bar{x}y + x\bar{y}$$

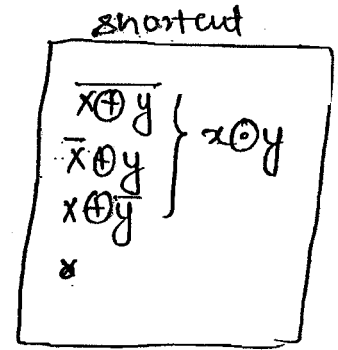


Shortcut (4)

$$\left\{ \begin{array}{l} x \oplus x = 0 \\ x \oplus \bar{x} = 1 \\ x \oplus 1 = \bar{x} \\ x \oplus 0 = x \end{array} \right. \uparrow$$

$$\begin{aligned} x \oplus 1 &= \bar{x} \cdot 1 + x \cdot \bar{1} \\ &= \bar{x} + x \cdot 0 \\ &= \bar{x} + 0 \\ &= \bar{x} \\ x \oplus 0 &= x \end{aligned}$$

⇒ workbook chapter 2: Q2, Q4

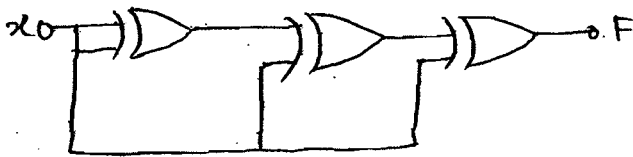Q2 for the circuit shown below the output F is given by:



- (a) F = 1
- ✓ (b) F = 0
- (c) F = x
- (d) F = \bar{x}

solⁿ

$$\left. \begin{array}{l} x \oplus x = 0 \text{ (o/p of gate 1)} \\ 0 \oplus x = x \text{ (o/p of gate 2)} \\ x \oplus x = 0 \text{ (o/p of gate 3)} \end{array} \right\} \therefore F = 0$$

Q4 consider the following boolean operators # with the following properties
 $x \# 0 = x$, $x \# 1 = \bar{x}$, $x \# x = 0$ and $x \# \bar{x} = 1$. Then

$x \# y$ is equivalent to:

(a) $x\bar{y} + \bar{x}y$ (b) $x\bar{y} + \bar{x}\bar{y}$ (c) $\bar{x}y + xy$ (d) $xy + \bar{x}\bar{y}$.

solⁿ $x \# y = x \oplus y = x\bar{y} + \bar{x}y$


⇒ EX-NOR: shortcut:

Shortcut (5)

$$\left\{ \begin{array}{l} x \odot x = 1 \\ x \odot \bar{x} = 0 \\ x \odot 1 = x \\ x \odot 0 = \bar{x} \end{array} \right.$$

⇒ workbook: CH2: Q17

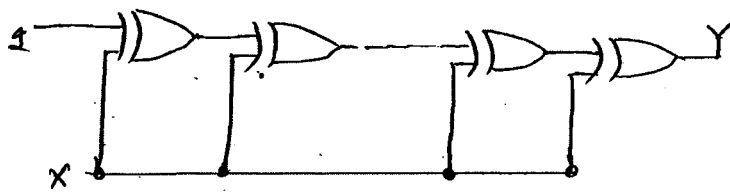Q17 If the input to the digital circuit of following circuit consisting of cascade of 20 XOR gates is x. then what is the output of Y?



- (a) 0
- (b) 1
- (c) x'
- (d) x

$1 \oplus x = \bar{x}$ (output of gate 1) \rightarrow odd no gate
 $x \oplus \bar{x} = 1$ (output of gate 2) \rightarrow even no gate

\therefore o/p of gate 19 = \bar{x}
 and o/p of gate 20 = 1
 $\therefore Y = 1$

\rightarrow for 2-variables:

EX-OR		
x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

$x \oplus y = x \odot y$
 $\overline{EX-OR} = EX-NOR$

EX-NOR		
x	y	$x \odot y$
0	0	1
0	1	0
1	0	0
1	1	1

\rightarrow for 3-variables:

EX-OR				
x	y	z	$x \oplus y$	$x \oplus y \oplus z$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

$\begin{matrix} 0 \rightarrow \text{same i/p} \\ 1 \rightarrow \text{diff i/p} \end{matrix}$

EX-NOR				
x	y	z	$x \odot y$	$x \odot y \odot z$
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

$\begin{matrix} 0 \rightarrow \text{diff i/p} \\ 1 \rightarrow \text{same i/p} \end{matrix}$

\curvearrowright EXNOR = EX-OR

\rightarrow conclusion:

for 2 variables,
 $x \oplus y = x \odot y$ i.e. $\overline{EX-OR} = EX-NOR$



for 3 variables,
 $x \oplus y \oplus z \neq x \odot y \odot z$ but $\overline{EX-OR} = EXNOR$

• for 4-variables,

$$w \oplus x \oplus y \oplus z = w \odot x \odot y \odot z. \quad \text{i.e. } \overline{\text{EX-OR}} = \text{EX-NOR}.$$

Hence,

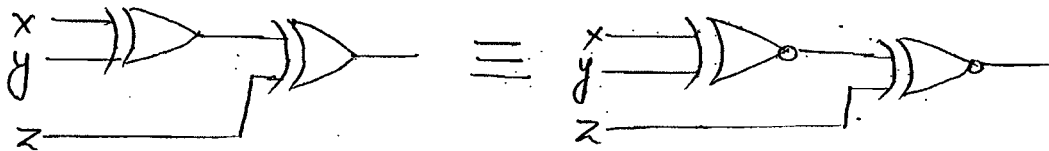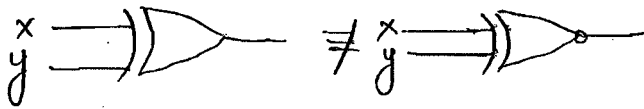$\overline{\text{EX-OR}} = \text{EX-NOR} \rightarrow$ for even variables $\text{EX-OR} = \text{EX-NOR} \rightarrow$ for odd variables
--




Note: two inputs EX-OR, EX-NOR gates are only available.

⇒ Logic minimization techniques:



- venn diagrams.
- Boolean algebra.
- Kmap.
- Tabulation method (i.e. clusky).

⇒ venn diagrams: (+ insight)

$A=0 \rightarrow$ unshaded

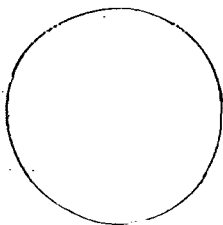

$A=1 \rightarrow$ shaded.

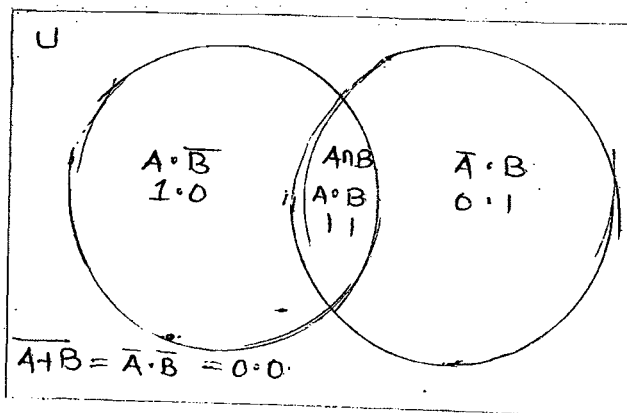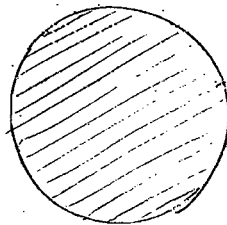


$A \cdot \bar{B} \rightarrow$ inhibition $\rightarrow A$ but not B

$\bar{A} \cdot B \rightarrow$ inhibition $\rightarrow B$ but not A .


$A \cap B \rightarrow A$ and $B \rightarrow A \cdot B$
 \hookrightarrow (AND gate)

①

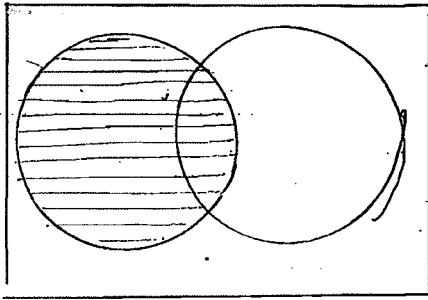


$$\begin{aligned}
 f &= A \cdot \bar{B} + A \cdot B \\
 &= A \cdot (\bar{B} + B) \\
 &= A \cdot (1) \\
 &= A
 \end{aligned}$$

②

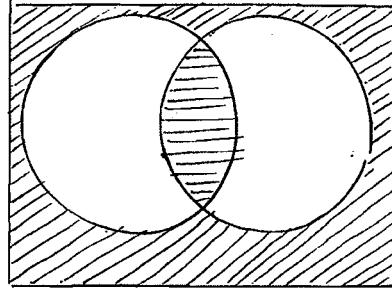



$$\begin{aligned}
 f &= A \cdot B + \bar{A} \cdot \bar{B} \\
 &\text{EX-NOR} \\
 &\text{unshaded region} \\
 &= f = \bar{A}B + A\bar{B} \\
 &= A \oplus B \\
 &= A \odot B
 \end{aligned}$$

③

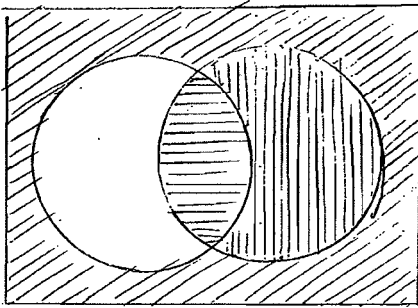


$$\begin{aligned}
 f &= A \cdot B + \bar{A} \cdot B + \bar{A} \cdot \bar{B} \\
 &= (A + \bar{A}) \cdot B + \bar{A} \cdot \bar{B} \\
 &= B(1) + \bar{A} \cdot \bar{B} \\
 &= B + \bar{A} \cdot \bar{B} \\
 &= B + \bar{A} = \bar{A} + B
 \end{aligned}$$
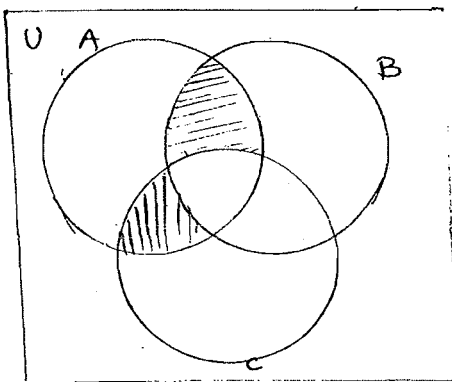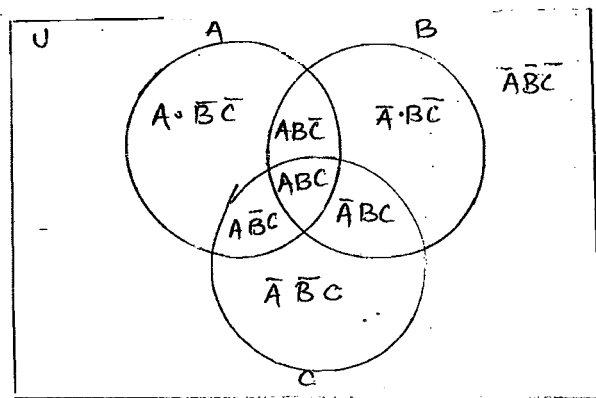
$$\begin{aligned}
 &\text{unshaded region} = \bar{A} \cdot \bar{B} \\
 &= \bar{A} + \bar{B} \\
 &= \overline{A + B} \\
 &\text{with } \bar{A} \cdot \bar{B} \text{ shaded area}
 \end{aligned}$$


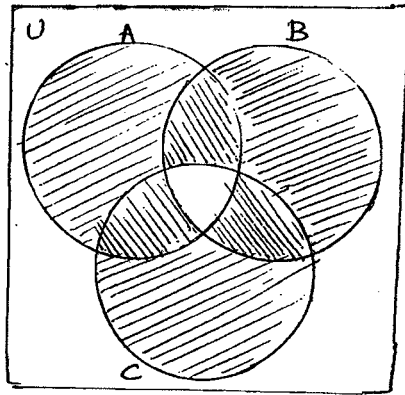
$$\begin{aligned}
 f &= A\bar{B}\bar{C} + \bar{A}\bar{B}C \\
 &= A(\bar{B}\bar{C} + \bar{B}C) \\
 &= A(B \oplus C)
 \end{aligned}$$



$$\text{shaded area} \Rightarrow f = A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + \bar{A}BC$$

$$\text{unshaded area} \Rightarrow \overline{\bar{A}\bar{B}\bar{C}} + ABC$$

⇒ functional completeness:

NAND, NOR } universal logic gates
 (Any function completely expressed by these gates).

$$\text{NAND} \rightarrow \text{AND} + \text{NOT}$$

$$\text{NOR} \rightarrow \text{OR} + \text{NOT}$$

{AND, NOT} → functionally completed

{OR, NOT} → functionally completed.

Eg: $f(A, B, C) = \bar{A} + B\bar{C}$ → checking of NOT operation

$$\begin{aligned} \rightarrow \{ \circ, \text{NOT} \} & \quad f(A, A, A) = A + A \cdot \bar{A} \\ & \quad = \bar{A} + 0 \\ & \quad = \bar{A} \rightarrow \text{NOT} \checkmark \end{aligned}$$

$$\{ +, \text{NOT} \}$$

similarly, $f(B, B, B) = \bar{B}$ and $f(C, C, C) = \bar{C}$

$$f(A, B, C) = \bar{A} + B \cdot \bar{C}$$

$$f(\bar{A}, B, \bar{B}) = \bar{\bar{A}} + B \cdot \bar{\bar{B}}$$

$$= A + B \cdot B$$

$$= A + B \rightarrow \text{'OR'} \checkmark$$

since we get {+, NOT}

∴ f is functionally completed.

$$\text{Eg: } f(A, B) = \bar{A} + B$$

$$\rightarrow f(A, A) = \bar{A} + A$$

$$= 1 \quad \text{NOT } \times$$

f is not functionally completed.

Hence, f is functionally incomplete