

Digital Electronics

Electronics: The study of motion of electron inside a semi-conductor is known as Electronics.


Note: there is a controlled conductivity in the case of semi-conductor

Gate: it is an electronic switching circuit made up of semi conductor switching devices.

Logic gates: Electronic switching ckt i.e gate with logical ideas implementation by Mr. boolean are logical gates.


Need of digital signal:

Disadvantages of analog signal:

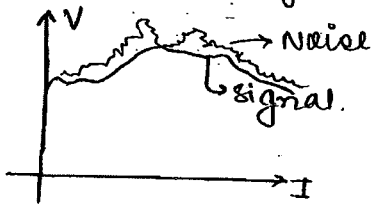

- (a) More bandwidth required.
- (b) More power consumption.
- (c) it is affected by noise more. (at receiving end if we amplify the signal, noise is also amplified)
- (d) no chance for encryption.


Advantages of digital signal:

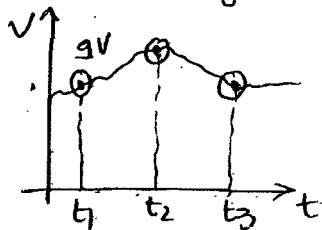

- (a) Less bandwidth required.
- (b) Less power consumption.
- (c) it is affected less by noise.
- (d) encryption is possible in digital signal.

Encryption is using digital data in the form of codes.

Block diagram:

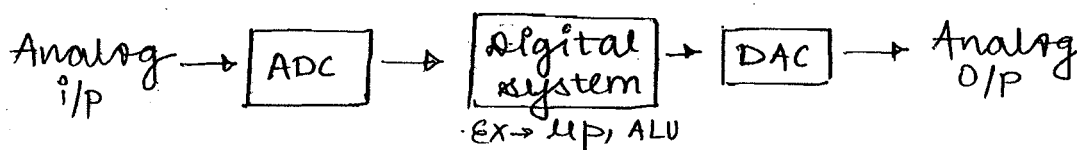

main systems:

- MP
- ALU
- computers
- calculators



subsystems:

- Registers
- flip
- counters
- flops



Building blocks:

- logic gates
- contains diodes,
- BJT, mosfet

SYLLABUS

Chapter 1: Basics:

- Boolean algebra
- Logic gates
- K-maps
- Number system
- Codes
- Data representation

Chapter 2: Combinational Circuits:

- Arithmetic circuits
 - half adder, half subtractor, full adder, full subtractor
 - parallel binary adder, look ahead carry adder
 - BCD adder, 2's complement adder subtractor
- Combinational circuits
 - Decoder, multiplexer, Demux, Encoder, decoder
 - comparator, code converter, parity generator, checker

Chapter 3: Sequential Circuits:


- Latches, flipflops, Registers, counters, state machines (mealy morel, moore model)

Chapter 4: Logic Families:

- RTL, DTL, HTL, TTL, ECL
- MOS logic: NMOS, PMOS, CMOS (mainly for Gate Exam)

Chapter 5: ADC and DAC conversions.

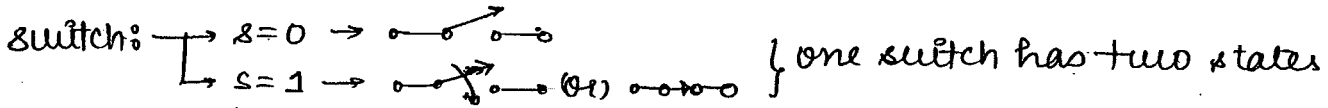Note: for 'n' switches we get 2^n possible states.



S_1	
0	OFF
1	ON

\Rightarrow two switches have four states.

Boolean logical ideas:

These are categorized into three ways:

- \rightarrow two functions that produce constant '0' or '1'. (Null, identity)
- \rightarrow four functions with unary operations; complementary and transfer \rightarrow (NOT) \rightarrow Buffer.
- \rightarrow ten functions with binary operations. (AND, OR, NAND, NOR, EX-OR, EX-NOR, Inhibition, Implication).

Note: for n input variables, we get (2^n) combinations and (2^{2^n}) possible functions.

Ex = n = 2 $\rightarrow 2^2 \rightarrow 4$ combinations.
 $\rightarrow 2^{2^2} \rightarrow 2^4 \rightarrow 16$ functions/operations.

Truth tables:

X	Y	Null	AND	$x \cdot \bar{y}$ inhibition transfer Buffer	$\bar{x} \cdot y$ transfer Buffer EX-OR	$x + y$	$\bar{x} + \bar{y}$	coincidence $x \oplus y$ EX-NOR	NOT	$\bar{x} + y$ implication	NOT	$\bar{x} + y$	NAND $\overline{(x \cdot y)}$	Identity			
		f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	0	1	1	0	0	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

$f_0 =$ Null operation

$f_1 = x \cdot y = x \cap y$ (AND)

$f_2 = x \cdot \bar{y} = x / y = (x \text{ but not } y) \Rightarrow$ inhibition.

$f_3 = x$ transfer \Rightarrow Buffer

$f_4 = \bar{x} \cdot y = y / x = (y \text{ but not } x) \Rightarrow$ inhibition.

$f_5 = y$ transfer \Rightarrow Buffer.

$f_6 = x \oplus y = \bar{x} \cdot y + x \cdot \bar{y} \Rightarrow$ EX-OR (for diff i/p \rightarrow o/p is high)

$f_7 = x + y = x \cup y$

$f_8 = \bar{x} + \bar{y} = x \downarrow y \Rightarrow$ NOR

$f_9 = x \odot y = \bar{x}y + x\bar{y} \Rightarrow$ when i/p same \rightarrow o/p is high
 \Rightarrow coincidence logic gate or Equivalence logic gate.

$f_{10} = \bar{y}$ = complementary = NOT gate.

$f_{11} = x + \bar{y} = x < y =$ if y then x \Rightarrow implication


$f_{12} = \bar{x}$ = complementary = NOT gate.

$f_{13} = \bar{x} + y = x > y =$ if x then y = implication

$f_{14} = \overline{(x \cdot y)} =$ NAND = $x \uparrow y$

$f_{15} = 1 =$ Identity.

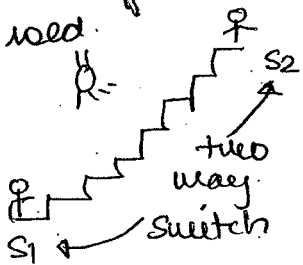note: for staircase and accelerator operation EX-OR logic gate is used.




S_2	S_1	bulb = $S_2 \oplus S_1$
0	0	0
0	1	1
1	0	1
1	1	0

\triangleright Basic logic gates: NOT, AND, OR


\triangleright combinational logic gates: NAND (AND NOT) & NOR (NOT OR)

\triangleright special purpose logic gates: EX-OR, EX-NOR (Arithmetic operations).

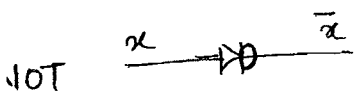• NAND & NOR are said to be universal logic gates.










NOT from NAND

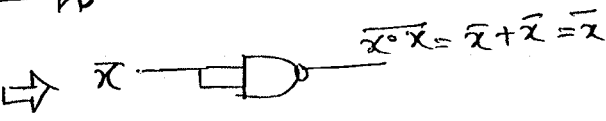


Demorgan's theorem.
 $\overline{x \cdot y} = (\bar{x} + \bar{y})$
 $\overline{x + y} = (\bar{x} \cdot \bar{y})$

\rightarrow symbols:

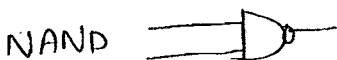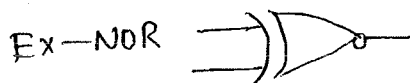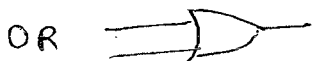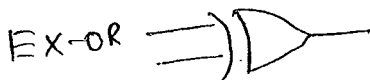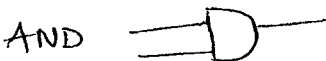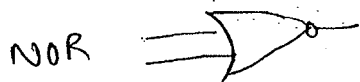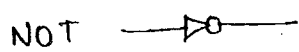

NOT from NOR

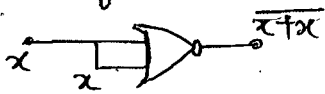

$$\Rightarrow \overline{x+x} = \overline{x \cdot \overline{x}} = \overline{x}$$

⊛ Shortcut: NO of Nand and NOR gate required:


Gate	NO of Nand gates	NO of NOR gates	NAND to NOR (OR)	NOR to NAND
→ NOT	1	1		
→ AND	2	3	(4)	(4)
→ OR	3	2		
→ EX-OR	4	5		
→ EX-NOR	5	4		

⊛ Design of logic gates using universal logic gates:
 • universal logic gates are NAND and NOR.

(a) NOT from NAND:

- output of NOT $\Rightarrow \overline{x}$
- NO of Nand gates req = 1

Circuit:

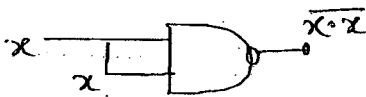


$$\rightarrow \overline{x \cdot x} = \overline{x} + \overline{x} \Rightarrow \overline{x}$$

(b) AND from NAND:

- output of AND $\Rightarrow x \cdot y$
- NO of NAND req = 2


Circuit

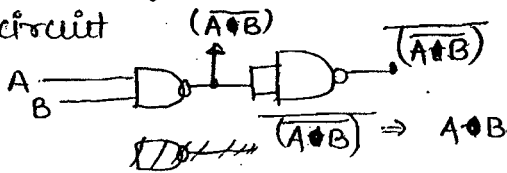

$$\overline{\overline{A \cdot B}} \Rightarrow A \cdot B$$

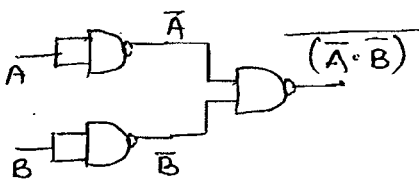(c) OR from NAND:

- output of OR $\Rightarrow x + y$
- NO of NAND $\Rightarrow 3$



$$\rightarrow \overline{\overline{A} \cdot \overline{B}} \Rightarrow \overline{\overline{A} + \overline{B}} = A + B$$

(d) NOT from NOR:

- output of NOT gate $= \overline{x}$
- NO of NOR gates req = 1


Circuit:



$$\rightarrow \overline{x+x} = \overline{x \cdot \overline{x}} = \overline{x}$$

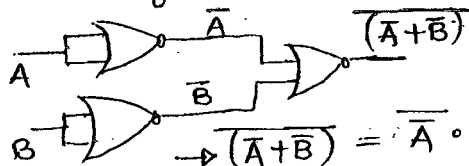(e) AND from NOR:


- output of AND $= x \cdot y$
- NO of NOR req = 3



$$\rightarrow \overline{\overline{A} + \overline{B}} = \overline{\overline{A} \cdot \overline{B}} = A \cdot B$$

(f) OR from NOR:

- output of OR $= x + y$
- NO of NOR = 2

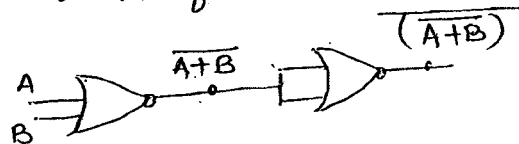


$$\rightarrow \overline{\overline{A + B}} = A + B$$

g) XOR from NAND: $(A \oplus B)$

→ output of EX-OR = $\bar{A}B + A\bar{B}$

→ no. of NAND = 4

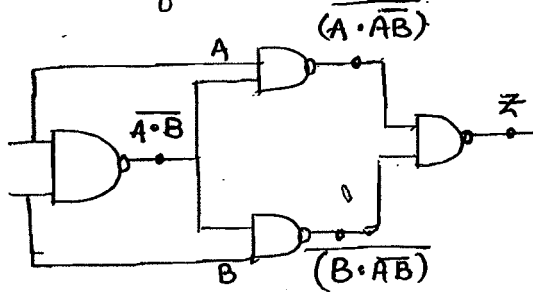

$$z = \overline{(A \cdot \bar{A}B) \cdot (B \cdot \bar{A}B)}$$

$$z = \overline{(A \cdot \bar{A}B) + (B \cdot \bar{A}B)}$$

$$z = A \cdot \bar{A}B + B \cdot \bar{A}B$$

$$z = A \cdot (\bar{A} + B) + B \cdot (\bar{A} + B)$$

$$z = A \cdot \bar{A} + A \cdot B + B \cdot \bar{A} + B \cdot B$$


$$z = A\bar{B} + B\bar{A}$$

$$z = A\bar{B} + \bar{A}B = A \oplus B$$

h) EX-NOR from NAND: $(A \odot B)$

→ output of EXNOR = $\bar{A}\bar{B} + AB$

→ no. of NAND req = 5

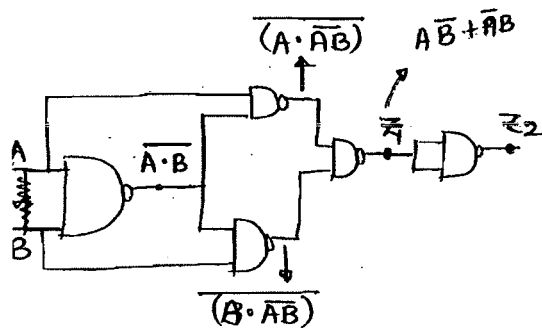

$$z_1 = A\bar{B} + \bar{A}B$$

$$z_2 = \bar{z}_1$$

$$= \overline{(A\bar{B} + \bar{A}B)}$$

$$= \overline{A\bar{B}} \cdot \overline{\bar{A}B}$$

$$= (\bar{A} + B)(A + \bar{B})$$

$$= \bar{A}(A + \bar{B}) + B(A + \bar{B})$$


$$= A\bar{A} + \bar{A}\bar{B} + BA + B\bar{B}$$

$$z_2 = \bar{A}\bar{B} + AB$$

(h) EX-OR from NOR:

→ output of EX-OR = $\bar{A}B + A\bar{B}$

→ no. of NOR = 5

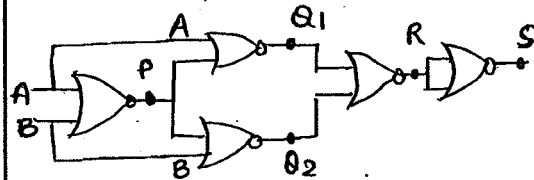

$$P = (\bar{A} + \bar{B})$$

$$Q_1 = (\bar{A} + P) = \overline{A + (\bar{A} + \bar{B})} = \bar{A} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{A} \cdot (A + B)$$

$$Q_2 = (\bar{B} + P) = \overline{B + (\bar{A} + \bar{B})} = \bar{B} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{B} \cdot (A + B)$$

$$R = (Q_1 + Q_2) = \overline{\bar{A} \cdot (A + B) + \bar{B} \cdot (A + B)}$$

$$= \overline{\bar{A}A + \bar{A}B + \bar{B}A + \bar{B}B} = \overline{\bar{A}B + \bar{B}A}$$


$$R = \overline{(\bar{A}B + \bar{B}A)}$$

$$S = \bar{R} = \overline{\overline{(\bar{A}B + \bar{B}A)}} = \bar{A}B + \bar{B}A$$

(j) EX-NOR from NOR:

→ output of EXNOR = $\bar{A}\bar{B} + AB$

→ no. of NOR = 4

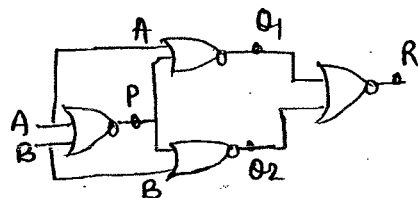

$$P = (\bar{A} + \bar{B})$$

$$Q_1 = (\bar{A} + P) = \overline{A + (\bar{A} + \bar{B})} = \bar{A} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{A} \cdot (A + B) = A\bar{A} + \bar{A}B = \bar{A}B$$

$$Q_2 = (\bar{B} + P) = \overline{B + (\bar{A} + \bar{B})} = \bar{B} \cdot (\overline{\bar{A} + \bar{B}})$$

$$= \bar{B} \cdot (A + B) = \bar{B}A + \bar{B}B = \bar{B}A$$

$$R = \overline{(\bar{A}B + \bar{B}A)}$$


$$= \overline{\bar{A}B} \cdot \overline{\bar{B}A}$$

$$= (\bar{A} + B) \cdot (\bar{B} + A)$$








$$= (\bar{A} + B) \cdot (\bar{A} + B)$$

$$= A(\bar{A} + B) + \bar{B}(\bar{A} + B)$$
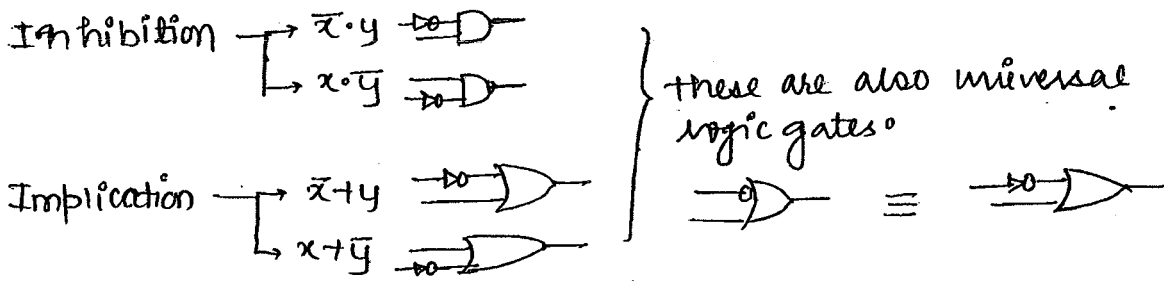
$$= A\bar{A} + AB + \bar{B}\bar{A} + \bar{B}B$$




switching circuits as logic gates:

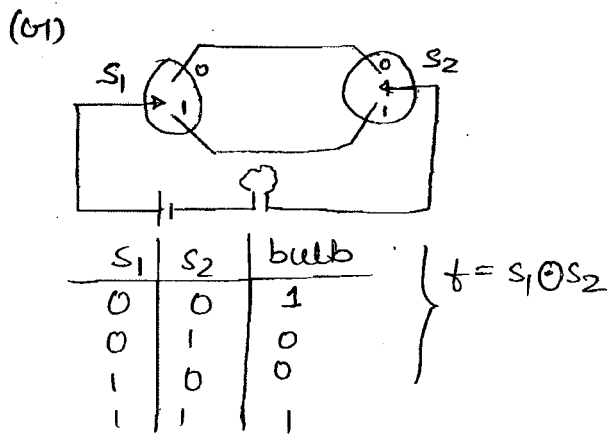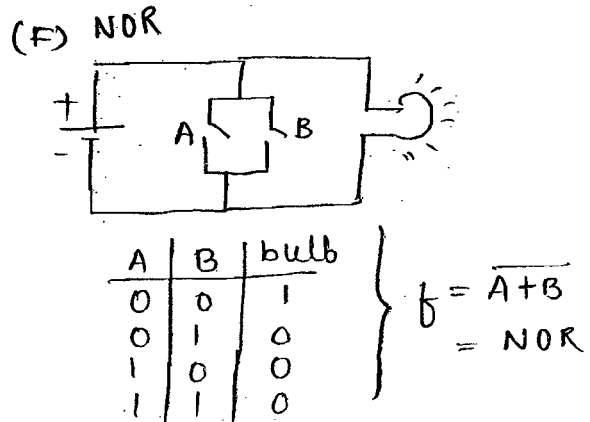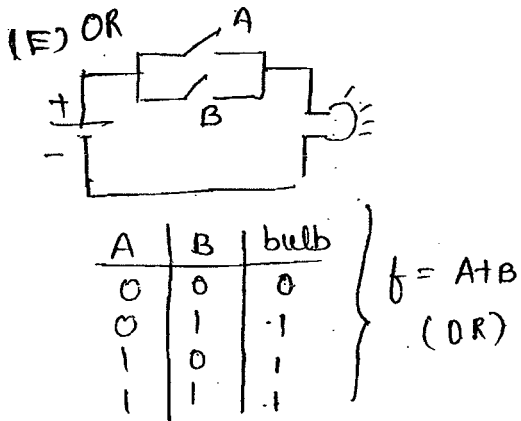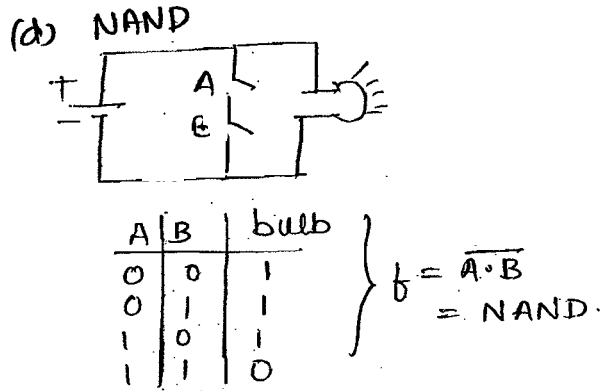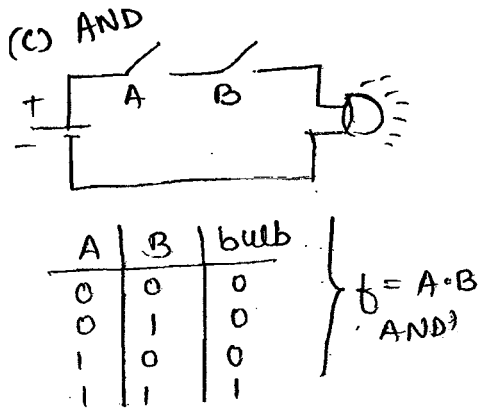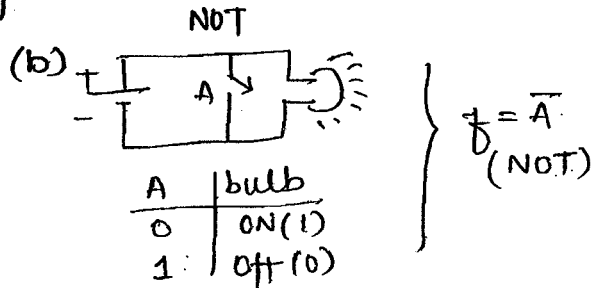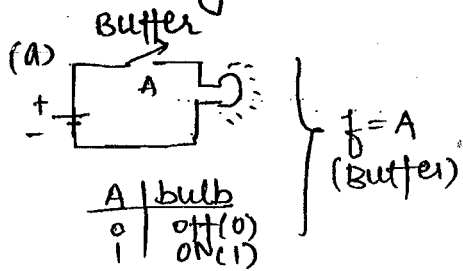


⇒ workbook practice : CH2 : Q T1, T2

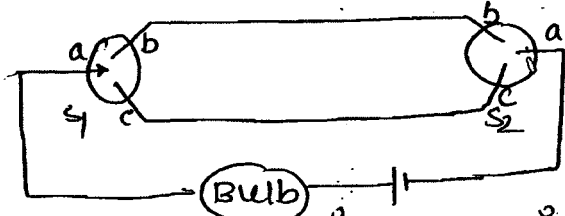Q1 A two way switch has three terminals a, b and c. In on position (logic value 1), a is connected to b, and in off position a is connected to c. Two of these switches are connected to bulb as shown in figure:



Which of the following expression, if true, will always result in lighting of bulb?

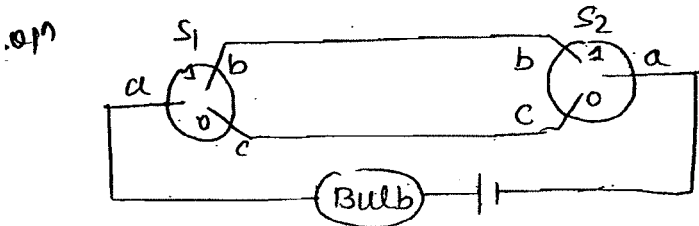- (a) $s_1 \cdot \bar{s}_2$ (b) $s_1 + s_2$ (c) $\overline{s_1 \oplus s_2}$ (d) $s_1 \oplus s_2$







s_1	s_2	bulb
0	0	1
0	1	0
1	0	0
1	1	1

} $s_1 \oplus s_2$

$s_1 \oplus s_2 = \overline{s_1 \oplus s_2}$

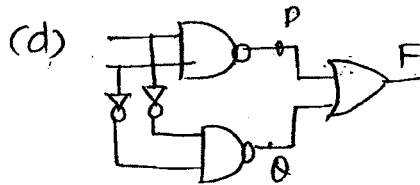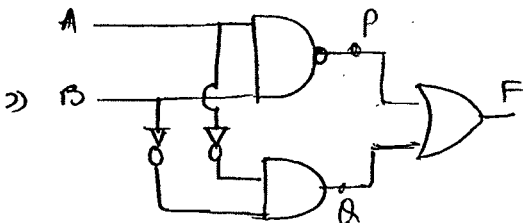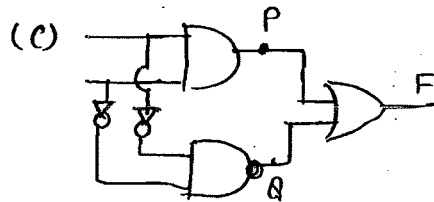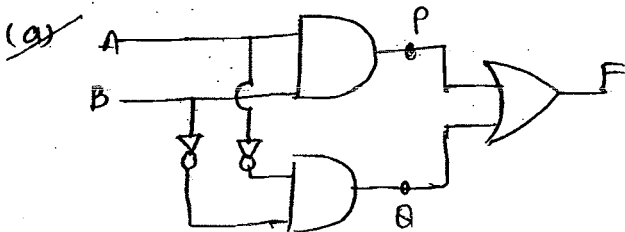Q2 which one of the following represents coincidence logic gate?




Q1) (a) truth table

A	B	P	Q	F
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

} $s_1 \oplus s_2 \rightarrow$ coincidence logic gate

Qex:

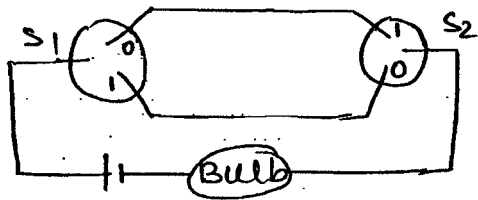

S1	S2	bulb
0	0	0
0	1	1
1	0	1
1	1	0

} $S_1 \oplus S_2$

* canonical forms:

x	y	min term	(product term)
m ₀	0	0	$\bar{x} \cdot \bar{y}$
m ₁	0	1	$\bar{x} \cdot y$
m ₂	1	0	$x \cdot \bar{y}$
m ₃	1	1	$x \cdot y$

$f(x,y) = \sum m(1,3)$
 $f = m_1 + m_3 = \bar{x} \cdot y + x \cdot y$
SOP
 $f = \sum m(1,3)$



x	y	max term	(sum term)
M ₀	0	0	$x + y$
M ₁	0	1	$x + \bar{y}$
M ₂	1	0	$\bar{x} + y$
M ₃	1	1	$\bar{x} + \bar{y}$

$f(x,y) = \prod M(0,2)$
 $f = M_0 \cdot M_2 = (x+y) \cdot (\bar{x} + \bar{y})$
POS
 $f = \prod M(0,2)$

$\Rightarrow \overline{\bar{x} \cdot \bar{y}} = \overline{\bar{x}} + \overline{\bar{y}}$
 $= x + y$

i.e. (min term) = (max term)

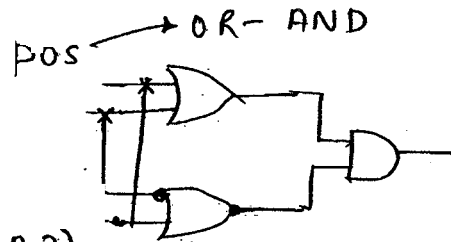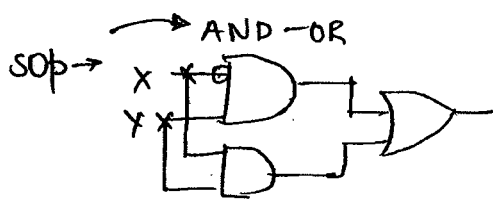$\left. \begin{aligned} \bar{m}_0 &= M_0 \\ \bar{m}_1 &= M_1 \\ \bar{m}_2 &= M_2 \\ \bar{m}_3 &= M_3 \end{aligned} \right\} \& \left. \begin{aligned} \bar{M}_0 &= m_0 \\ \bar{M}_1 &= m_1 \\ \bar{M}_2 &= m_2 \\ \bar{M}_3 &= m_3 \end{aligned} \right\}$



$f = \sum m(1,3) = \prod M(0,2)$
missing no. ↑

Q

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

SOP = ?
 POS = ?

$\left. \begin{aligned} \text{SOP}(f) &= \bar{x}y + x\bar{y} \\ \text{POS}(f) &= (\bar{x} + \bar{y}) \cdot (x + y) \end{aligned} \right\} \text{This is EX-OR gate}$

$= \bar{x}(x+y) + \bar{y}(x+y)$
 $= \bar{x}\bar{x} + \bar{x}y + \bar{y}x + \bar{y}\bar{y}$
 $= \bar{x}y + x\bar{y} = x \oplus y$

• In canonical sop. form, each product term must contains all variable of given expression.
 Note: In canonical sop, each product term is known as min term.

• In canonical pos, each sum term is known as max term.

Pos: $f = \pi M(1, 3) \rightarrow$ ~~canon~~ standard form.

$$= M_1 + M_3$$

$$f = x\bar{y} + x\bar{y} \rightarrow \text{canonical form.}$$

$$= \bar{y}(x + \bar{x})$$

$$f = \bar{y} \rightarrow \text{minimal form.}$$

① If more zero's is given in output function then we go for min term with (1)

If more 1's are given in output function then we go for max term with (0).

$$f = \sum m(1, 5) = \pi M(0, 2, 3, 4, 6, 7)$$


$\rightarrow 101 \rightarrow n=3 \rightarrow 2^3 = 8 \text{ combinations}$

$$= \pi M(1, 9) = \sum m(0, 2, 3, 4, 5, 6, 7, 8, 9, 11, 12, 13, 14, 15)$$

1001
 \downarrow
 $n=4$
 $\hookrightarrow 2^4 = 16 \text{ combinations}$

Ex: $f_1 = \sum m(0, 1, 2, 4)$
 $f_2 = \sum m(1, 3, 4, 5)$
 $f_3 = \sum m(2, 3, 4, 5, 6, 7)$

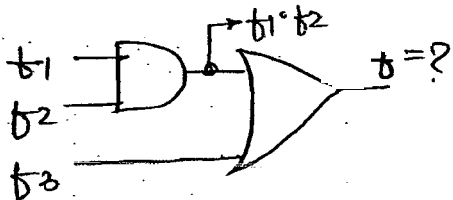
AND = $f_1 \cdot f_2 = f_1 \cap f_2$
 OR = $f_1 + f_2 = f_1 \cup f_2$



$f_1 \cdot f_2 = \sum m(1, 4)$
 $f_3 = \sum m(2, 3, 4, 5, 6, 7)$

$f \Rightarrow$
 $f_1 \cdot f_2 = \sum m(1, 2, 3, 4, 5, 6, 7)$
 $\neq f_3$

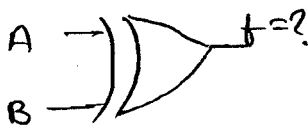Ex: $A = \sum m(0, 1, 4, 5)$
 $B = \sum m(2, 3, 4, 5, 6, 7)$



$f = A \oplus B$
 $= \bar{A}\bar{B} + A\bar{B} + \bar{A}B + AB$
 $= (\bar{A} + B)A + (\bar{A} \cdot B)$
 \neq

$\bar{A}B \rightarrow$ inhibition $\rightarrow B$ but not A .
 $\bar{A}B = \sum m(2, 3, 6, 7)$




$A\bar{B} \rightarrow$ inhibition $\rightarrow A$ but not B .
 $A\bar{B} = \sum m(0, 1)$

$\bar{A}B + A\bar{B} = \sum m(0, 1, 2, 3, 6, 7)$

workbook practice: CH2: Q 2)

Q1 A universal logic gate can be implemented any boolean function by connecting sufficient no. of them appropriately.

Three gates shown:

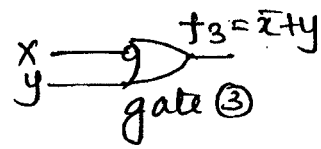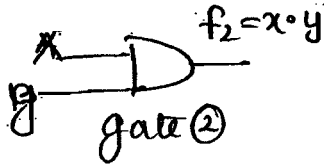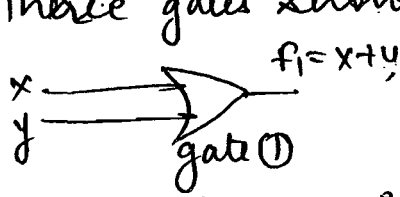


Which of the following is correct statement?

- (a) Gate 1 is a universal gate.
- (b) Gate 2 is a universal gate.
- (c) Gate 3 is a universal gate.
- (d) Gate none of the gates are universal gate.



soln) Gate 1: $f_1 = x + y \rightarrow$ it is OR gate \rightarrow not universal.

Gate 2: $f_2 = x \cdot y \rightarrow$ it is AND gate \rightarrow not universal.

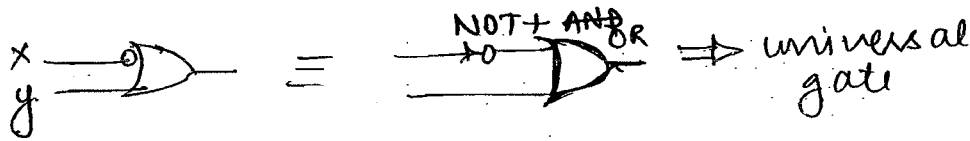Gate 3: $f_3 = \bar{x} + y \rightarrow$ implication \rightarrow universal gate.




Alternative logic gates:

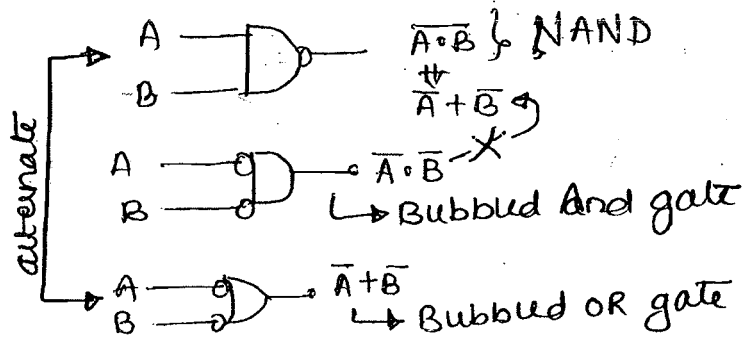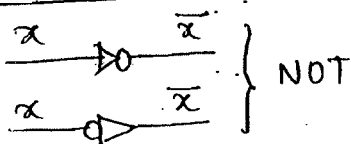

- NAND $\xrightarrow{\text{alternate}}$ Bubbled OR gate
 - NOR $\xrightarrow{\text{alternate}}$ Bubbled And gate
 - AND $\xrightarrow{\text{alternate}}$ Bubbled NOR gate
 - OR $\xrightarrow{\text{alternate}}$ Bubbled NAND gate
- shortcut

⇒ workbook practice: CH2: Q3, Q1, Q12

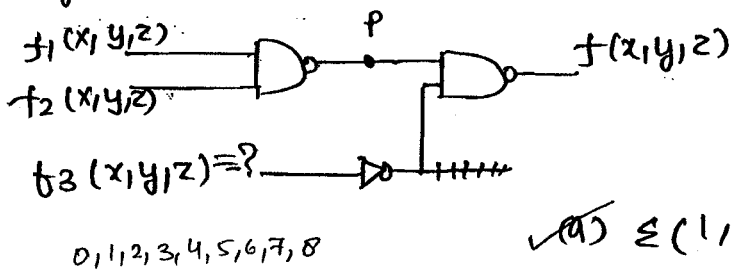Q3 consider the following logic circuit whose inputs are functions f_1, f_2 and f_3 and output is f . given that:



$$f_1(x,y,z) = \sum(0,1,3,5)$$

$$f_2(x,y,z) = \sum(6,5)$$

$$f(x,y,z) = \sum(1,4,5)$$

f_3 is

0,1,2,3,4,5,6,7,8

✓ (a) $\sum(1,4,5)$

(b) $\sum(6,7)$

(c) $\sum(0,1,3,5)$

(d) None.



Solⁿ

$$P = \overline{f_1 \cdot f_2} = \overline{f_1} + \overline{f_2}$$

$$= \sum(2,4,6,7,8) + \sum(1,2,3,4,7,8)$$

$$= \sum(1,2,3,4,6,7,8)$$

X

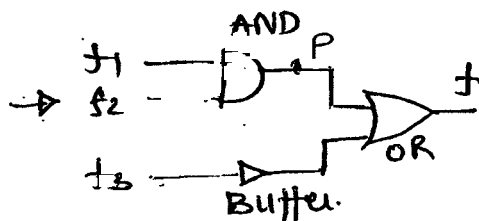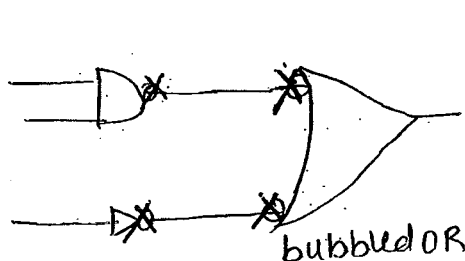

$$P = f_1 \cdot f_2 = f_1 \cap f_2$$

$$P = \sum m(5)$$

$$f_3 = \sum m(1,4,5)$$

$$f = P \cup f_3$$

$$\sum m(1,4,5) = \sum m(5) \cup \sum m(\text{---})$$

$$\therefore f_3 = \sum m(1,4,5) \text{ or } \sum m(1,4)$$

Q1 consider the following SOP expression F;

$$F = ABC + \overline{A}\overline{B}C + A\overline{B}C + \overline{A}BC + \overline{A}\overline{B}\overline{C}$$

the equivalent ~~sum of product~~ product of sum expression is:

✓ (a) $F = (A+B+C) (\overline{A}+B+C) (\overline{A}+\overline{B}+C)$

(b) $F = (A+\overline{B}+\overline{C}) (A+B+C) (\overline{A}+\overline{B}+\overline{C})$

(c) $F = (\overline{A}+B+\overline{C}) (A+\overline{B}+\overline{C}) (A+B+C)$

(d) $F = (\overline{A}+\overline{B}+C) (A+B+\overline{C}) (A+B+C)$